


# ***Circuit Analysis Procedure***

# Overview

- **Important concept – analyze digital circuits**
  - **Given a circuit**
    - **Create a truth table**
    - **Create a minimized circuit**
- **Approaches**
  - **Boolean expression approach**
  - **Truth table approach**
- **Leads to minimized hardware**
- **Provides insights on how to design hardware**
  - **Tie in with K-maps (next time)**

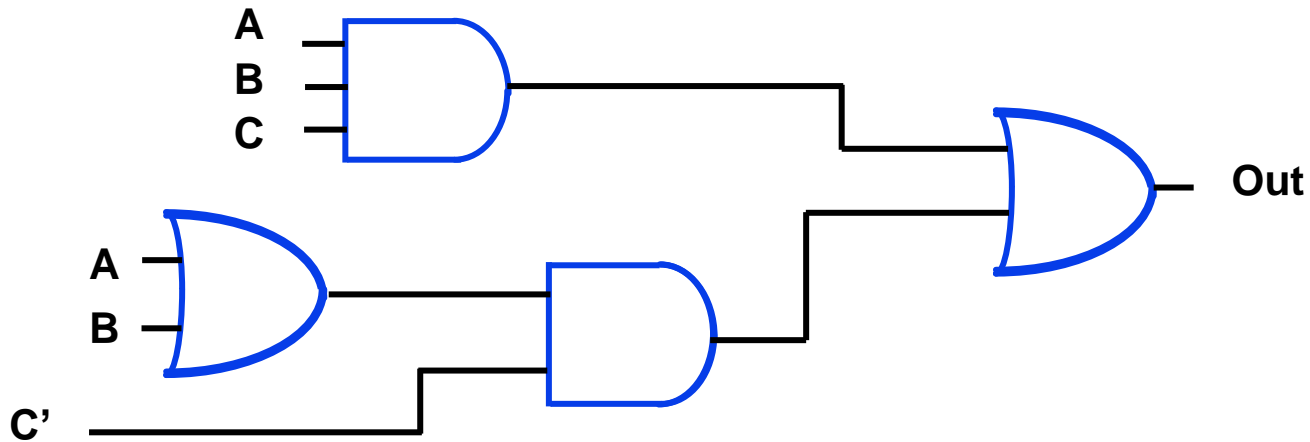
# The Problem

- How can we convert from a circuit drawing to an equation or truth table?
- Two approaches
  - Create intermediate equations
  - Create intermediate truth tables




# Label Gate Outputs

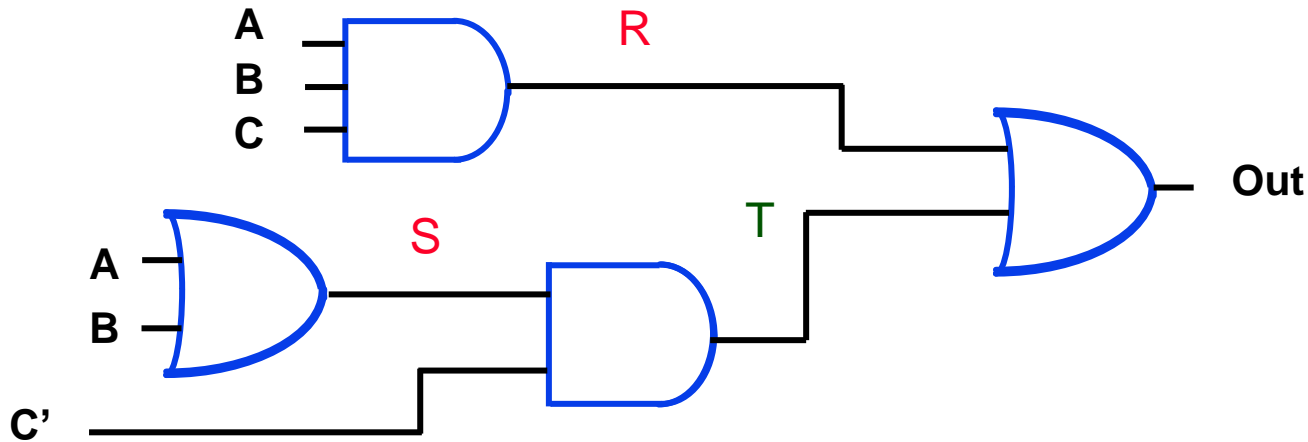1. Label all gate outputs that are a function of input variables.
2. Label gates that are a function of input variables and previously labeled gates.
3. Repeat process until all outputs are labelled.



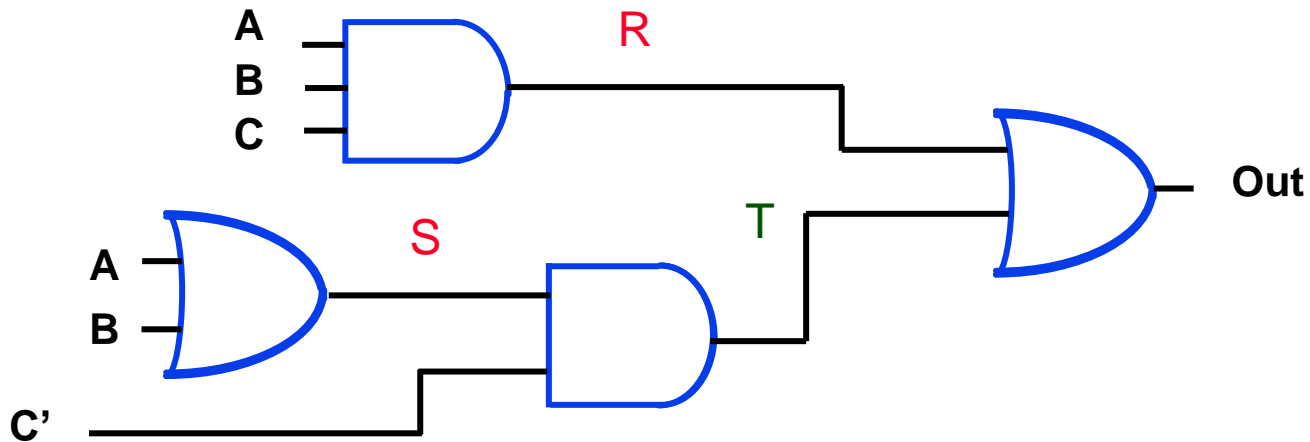
# Approach 1: Create Intermediate Equations

- ❑ Step 1: Create an equation for each gate output based on its input.
  - $R = ABC$
  - $S = A + B$
  - $T = C'S$
  - $Out = R + T$



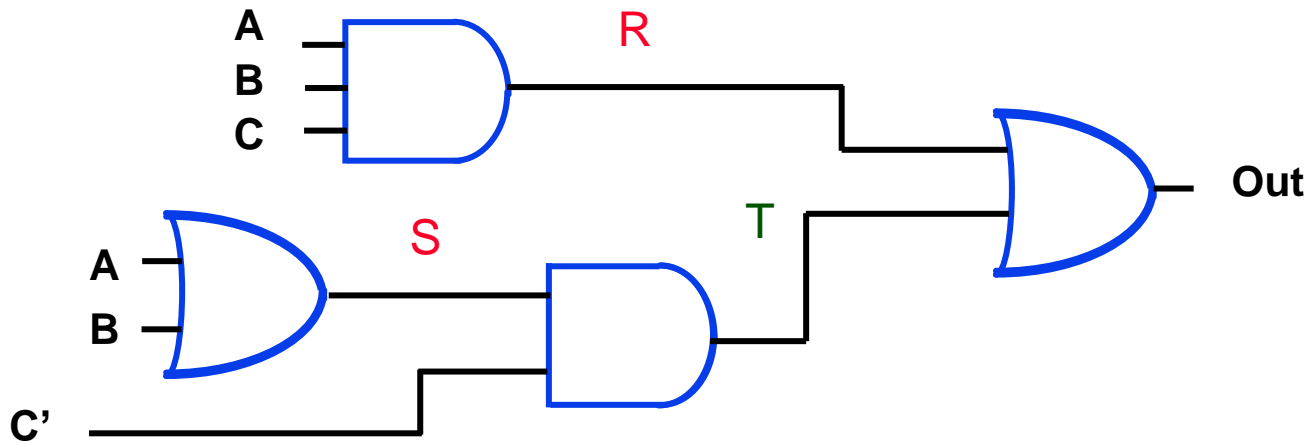
# Approach 1: Substitute in subexpressions

- Step 2: Form a relationship based on input variables (A, B, C)
  - $R = ABC$
  - $S = A + B$
  - $T = C'S = C'(A + B)$
  - $\text{Out} = R + T = ABC + C'(A + B)$


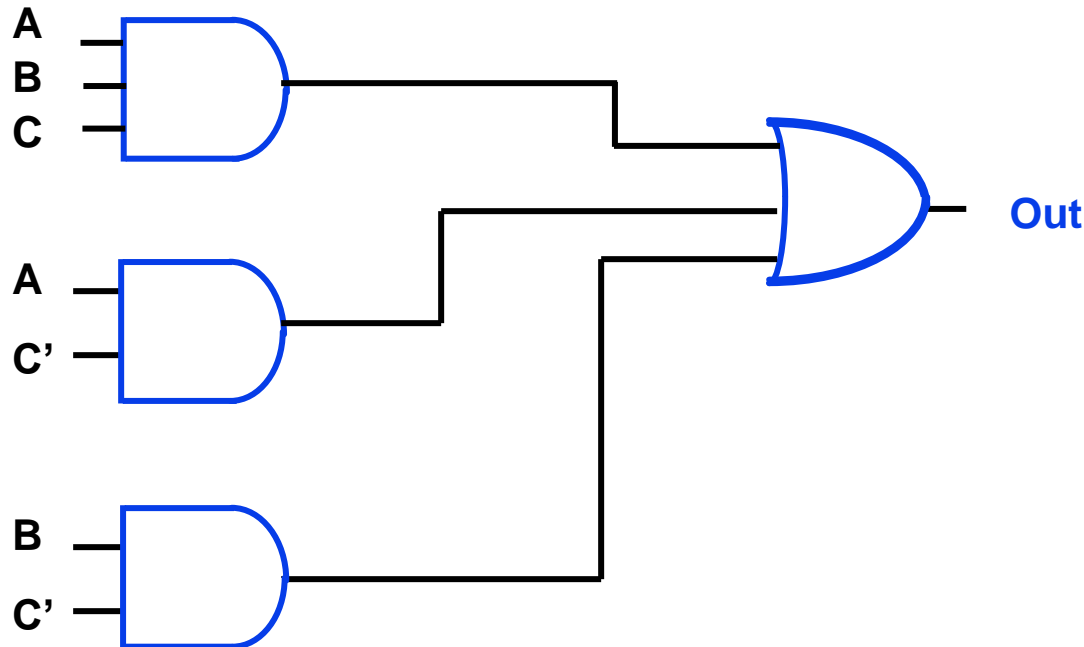
# Approach 1: Substitute in subexpressions


- ❑ Step 3: Expand equation to SOP final result
  - **Out =  $ABC + C'(A+B) = ABC + AC' + BC'$**



# Approach 2: Truth Table

- Step 1: Determine outputs for functions of input variables.

A	B	C	R	S
0	0	0	0	0
0	0	1	0	0
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

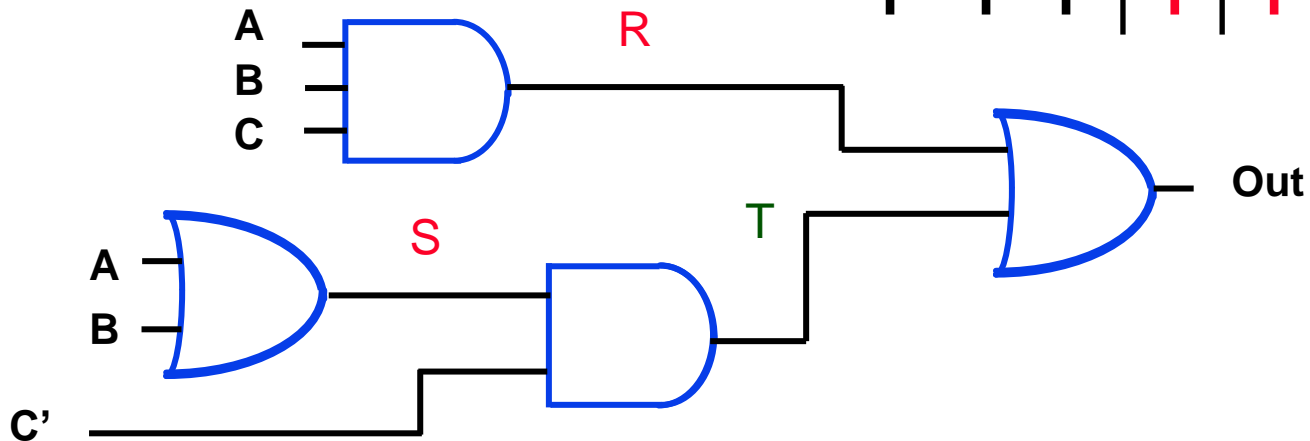




## Approach 2: Truth Table

- Step 2: Determine outputs for functions of intermediate variables.

$$T = S * C'$$

A	B	C	C'	R	S	T
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	1	1
0	1	1	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	0	1	0
1	1	0	1	0	1	1
1	1	1	0	1	1	0

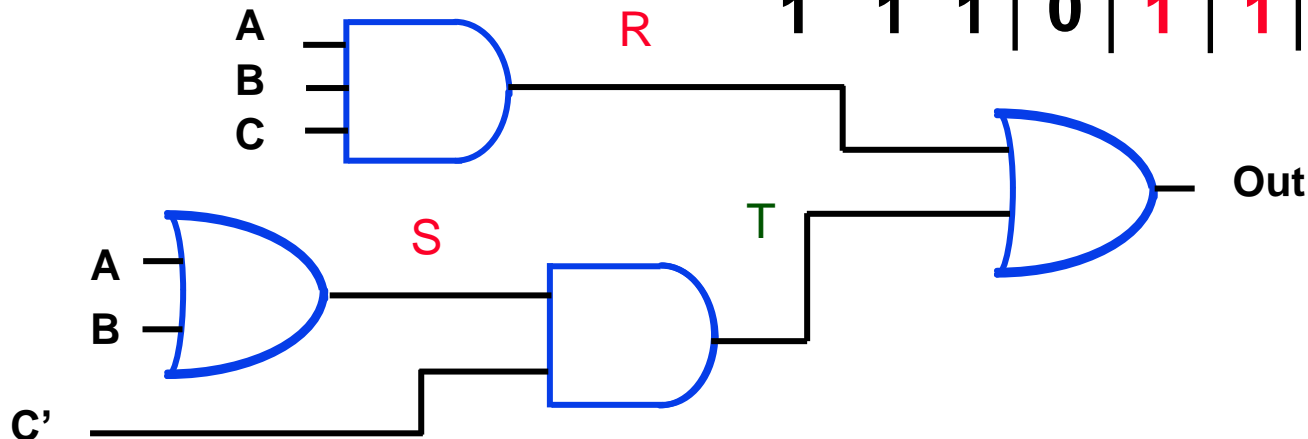


## Approach 2: Truth Table

- Step 3: Determine outputs for function.

$$R + T = \text{Out}$$

A	B	C	R	S	T	Out
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	0	1	1	1
1	1	1	1	1	0	1

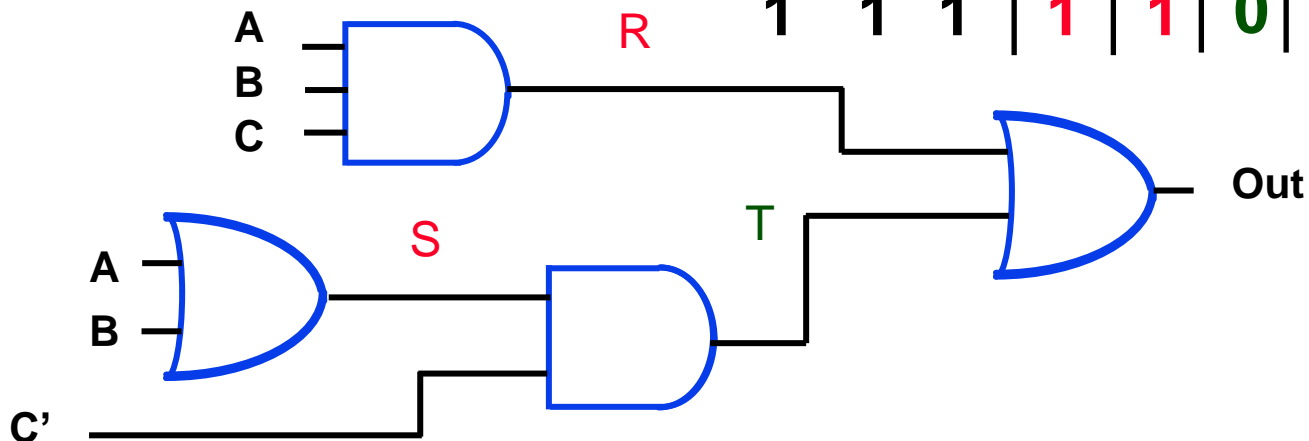

# More Difficult Example

## □ Step 3: Note labels on interior nodes

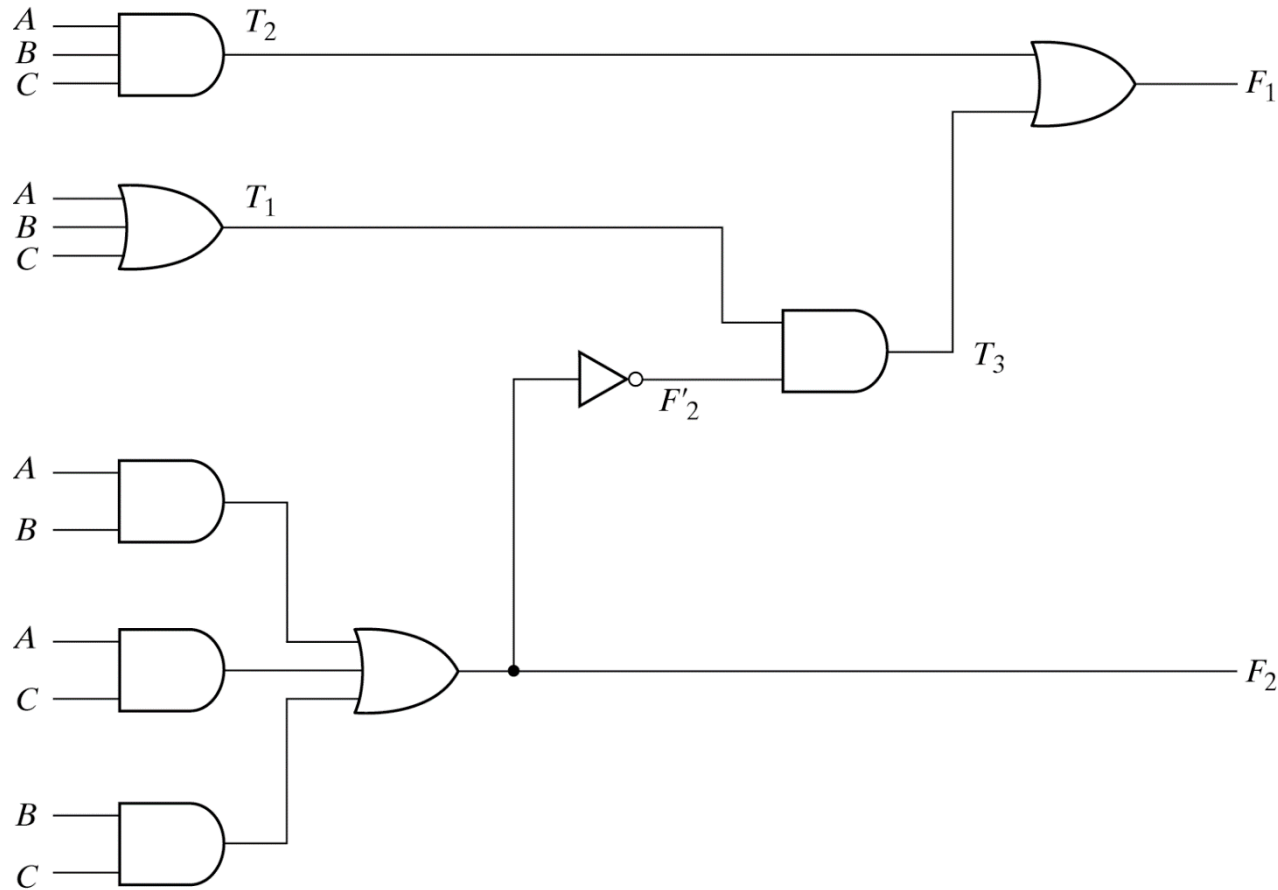


Fig. 4-2 Logic Diagram for Analysis Example

# More Difficult Example: Truth Table

- ❑ Remember to determine intermediate variables starting from the inputs.
- ❑ When all inputs determined for a gate, determine output.
- ❑ The truth table can be reduced using K-maps.

A	B	C	$F_2$	$F'_2$	$T_1$	$T_2$	$T_3$	$F_1$
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

# Summary

- **Important to be able to convert circuits into truth table and equation form**
  - **WHY? ---- leads to minimized sum of product representation**
- **Two approaches illustrated**
  - **Approach 1: Create an equation with circuit output dependent on circuit inputs**
  - **Approach 2: Create a truth table which shows relationship between circuit inputs and circuit outputs**
- **Both results can then be minimized using K-maps.**
- **Next time: develop a minimized SOP representation from a high level description**