

Binary Adders and Subtractors


Overview

- **Addition and subtraction of binary data is fundamental**
 - Need to determine hardware implementation
- **Represent inputs and outputs**
 - Inputs: single bit values, carry in
 - Outputs: Sum, Carry
- **Hardware features**
 - Create a single-bit adder and chain together
- **Same hardware can be used for addition and subtraction with minor changes**
- **Dealing with overflow**
 - What happens if numbers are too big?

Half Adder

- **Add two binary numbers**
 - A_0 , B_0 -> single bit inputs
 - S_0 -> single bit sum
 - C_1 -> carry out

A_0	B_0	S_0	C_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Dec Binary

1	1
+1	+1
<hr/>	
2	10

Multiple-bit Addition

- Consider single-bit adder for each bit position.

$$\begin{array}{rcccc} & A_3 & A_2 & A_1 & A_0 \\ \mathbf{A} & 0 & 1 & 0 & 1 \end{array}$$

$$\begin{array}{rcccc} & B_3 & B_2 & B_1 & B_0 \\ \mathbf{B} & 0 & 1 & 1 & 1 \end{array}$$

$$\begin{array}{rcccc} & 1 & 1 & 1 & \\ \mathbf{A} & 0 & 1 & 0 & 1 \\ \mathbf{B} & 0 & 1 & 1 & 1 \\ \hline & 1 & 1 & 0 & 0 \end{array}$$

$$\begin{array}{r} C_{i+1} \leftarrow \\ C_i \\ A_i \\ + B_i \\ \hline S_i \end{array}$$

Each bit position creates a sum and carry

Full Adder

- Full adder includes carry in C_i
- Notice interesting pattern in Karnaugh map.

C_i	A_i	B_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		$A_i B_i$			
		00	01	11	10
C_i	0		1		1
	1	1		1	

S_i

Full Adder

- Full adder includes carry in C_i
- Alternative to XOR implementation

C_i	A_i	B_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned} S_i &= !C_i \& !A_i \& B_i \\ &\# !C_i \& A_i \& !B_i \\ &\# C_i \& !A_i \& !B_i \\ &\# C_i \& A_i \& B_i \end{aligned}$$

Full Adder

- **Reduce and/or representations into XORs**

$$\begin{aligned} S_i &= !C_i \& !A_i \& B_i \\ &\# !C_i \& A_i \& !B_i \\ &\# C_i \& !A_i \& !B_i \\ &\# C_i \& A_i \& B_i \end{aligned}$$

$$\begin{aligned} S_i &= !C_i \& (!A_i \& B_i \# A_i \& !B_i) \\ &\# C_i \& (!A_i \& !B_i \# A_i \& B_i) \end{aligned}$$

$$\begin{aligned} S_i &= !C_i \& (A_i \$ B_i) \\ &\# C_i \& !(A_i \$ B_i) \end{aligned}$$

$$S_i = C_i \$ (A_i \$ B_i)$$

Full Adder

- Now consider implementation of carry out
- Two outputs per full adder bit (C_{i+1} , S_i)

C_i	A_i	B_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$A_i B_i$		00	01	11	10
C_i	0			1	
	1		1	1	1

C_{i+1}

Note: 3 inputs

Full Adder

- Now consider implementation of carry out
- Minimize circuit for carry out - C_{i+1}

C_i	A_i	B_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$A_i B_i$		00	01	11	10
C_i	0			1	
	1		1	1	1

C_{i+1}

$$\begin{aligned} C_{i+1} = & A_i \ \& \ B_i \\ & \# \ C_i \ \& \ B_i \\ & \# \ C_i \ \& \ A_i \end{aligned}$$

Full Adder

$$\begin{aligned} C_{i+1} &= A_i \& B_i \\ &\# C_i \& !A_i \& B_i \\ &\# C_i \& A_i \& !B_i \end{aligned}$$

$$\begin{aligned} C_{i+1} &= A_i \& B_i \\ &\# C_i \& (!A_i \& B_i \# A_i \& !B_i) \end{aligned}$$

$$C_{i+1} = A_i \& B_i \# C_i \& (A_i \$ B_i)$$

Recall:

$$S_i = C_i \$ (A_i \$ B_i)$$


$$C_{i+1} = A_i \& B_i \# C_i \& (A_i \$ B_i)$$

Full Adder

- Full adder made of several half adders


$$S_i = C_i \oplus (A_i \oplus B_i)$$
 
$$C_{i+1} = A_i \& B_i \# C_i \& (A_i \oplus B_i)$$



Full Adder

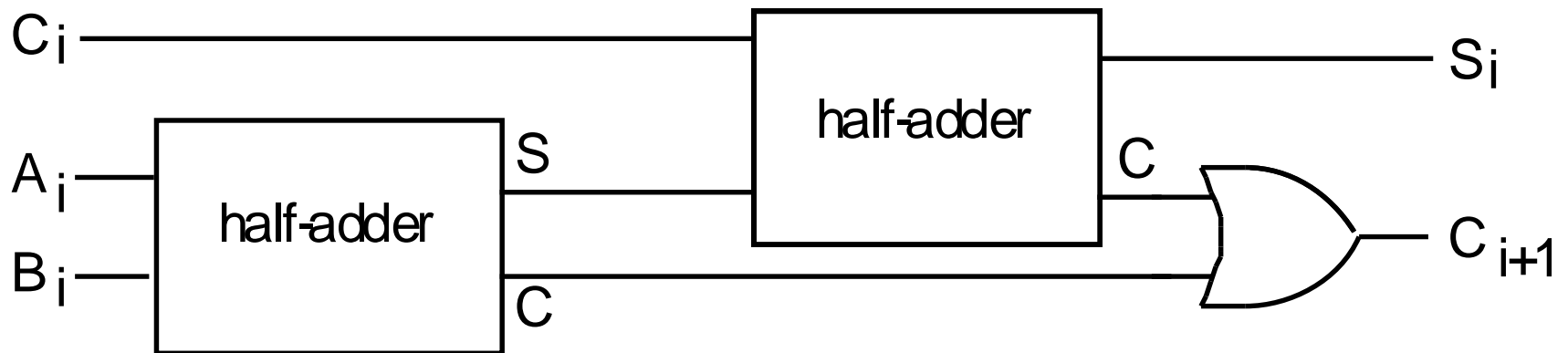
- Hardware repetition simplifies hardware design



A full adder can be made from two half adders (plus an OR gate).

Full Adder

 
- **Putting it all together**
 - Single-bit full adder
 - Common piece of computer hardware



Block Diagram

4-Bit Adder

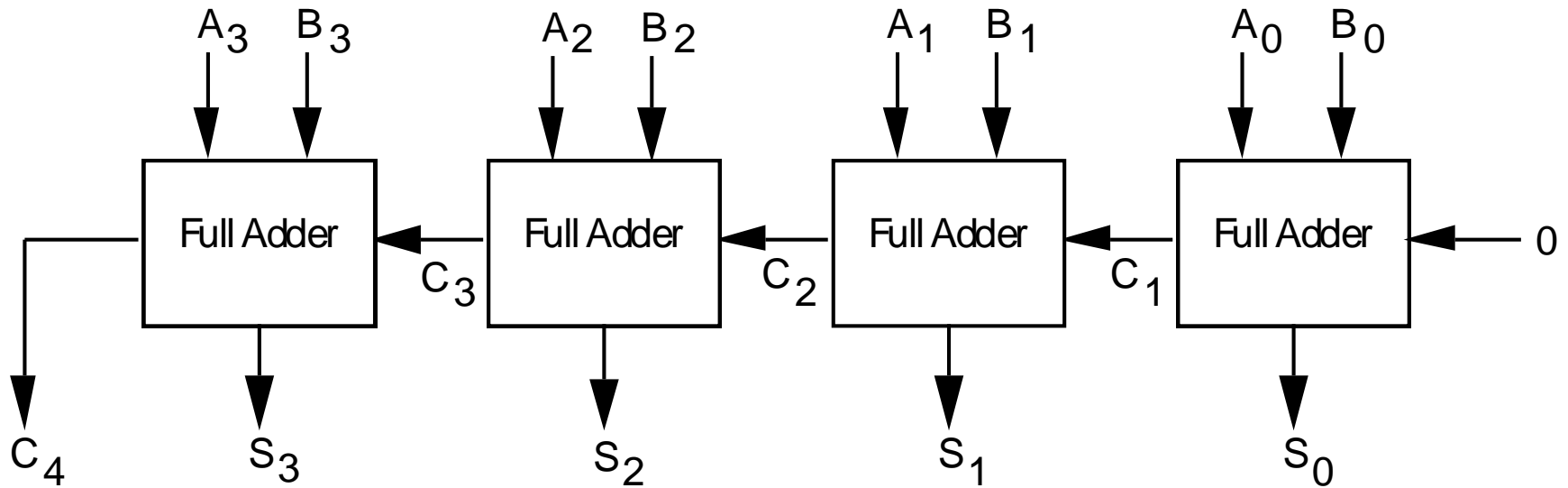- Chain single-bit adders together.
- What does this do to delay?



C	1	1	1	0
A	0	1	0	1
B	0	1	1	1
<hr/>				
S	1	1	0	0


Negative Numbers – 2's Complement.

- **Subtracting a number is the same as:**
 1. Perform 2's complement
 2. Perform addition
- **If we can augment adder with 2's complement hardware?**

$$\begin{aligned} 1_{10} &= 01_{16} = 00000001 \\ -1_{10} &= FF_{16} = 11111111 \end{aligned}$$


$$\begin{aligned} 128_{10} &= 80_{16} = 10000000 \\ -128_{10} &= 80_{16} = 10000000 \end{aligned}$$

4-bit Subtractor: $E = 1$

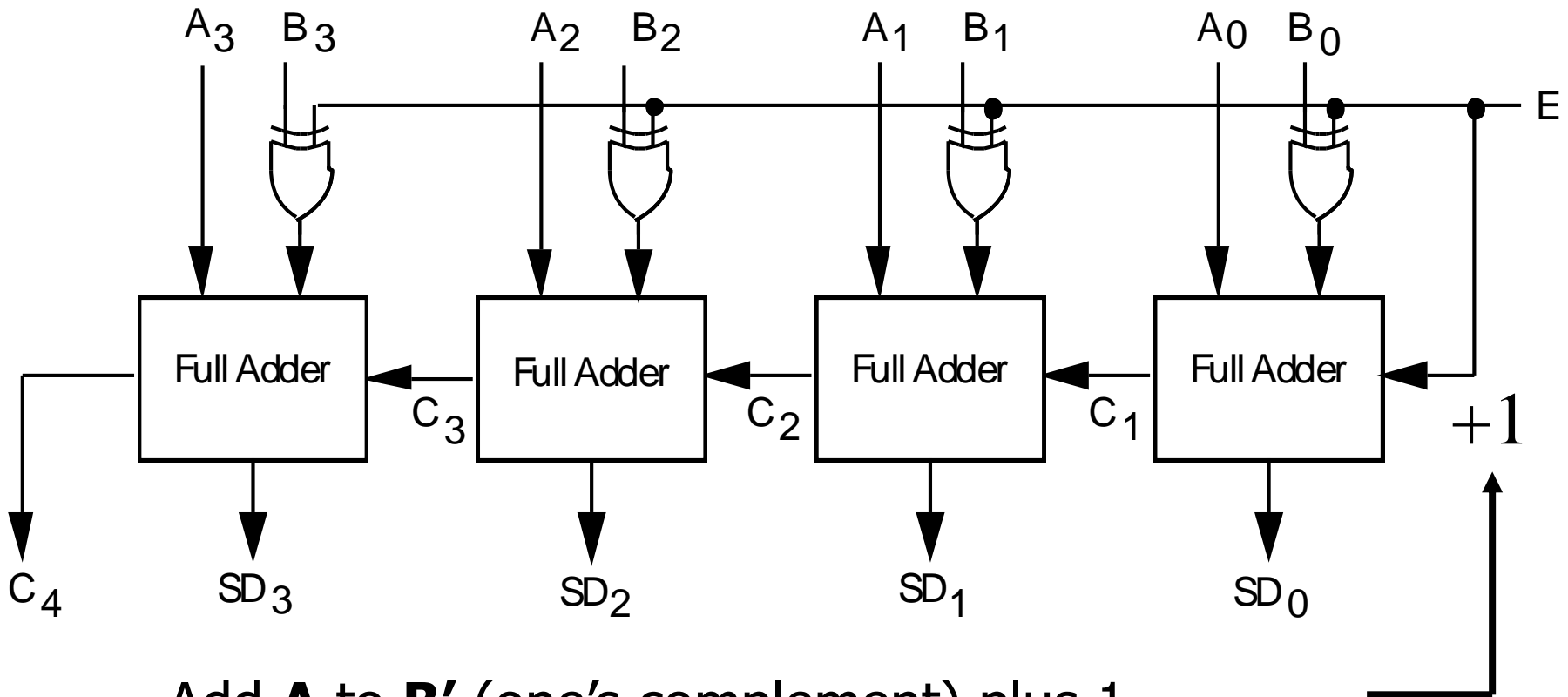

Add **A** to **B'** (one's complement) plus 1
That is, add **A** to two's complement of **B**
D = A - B


Adder- Subtractor Circuit

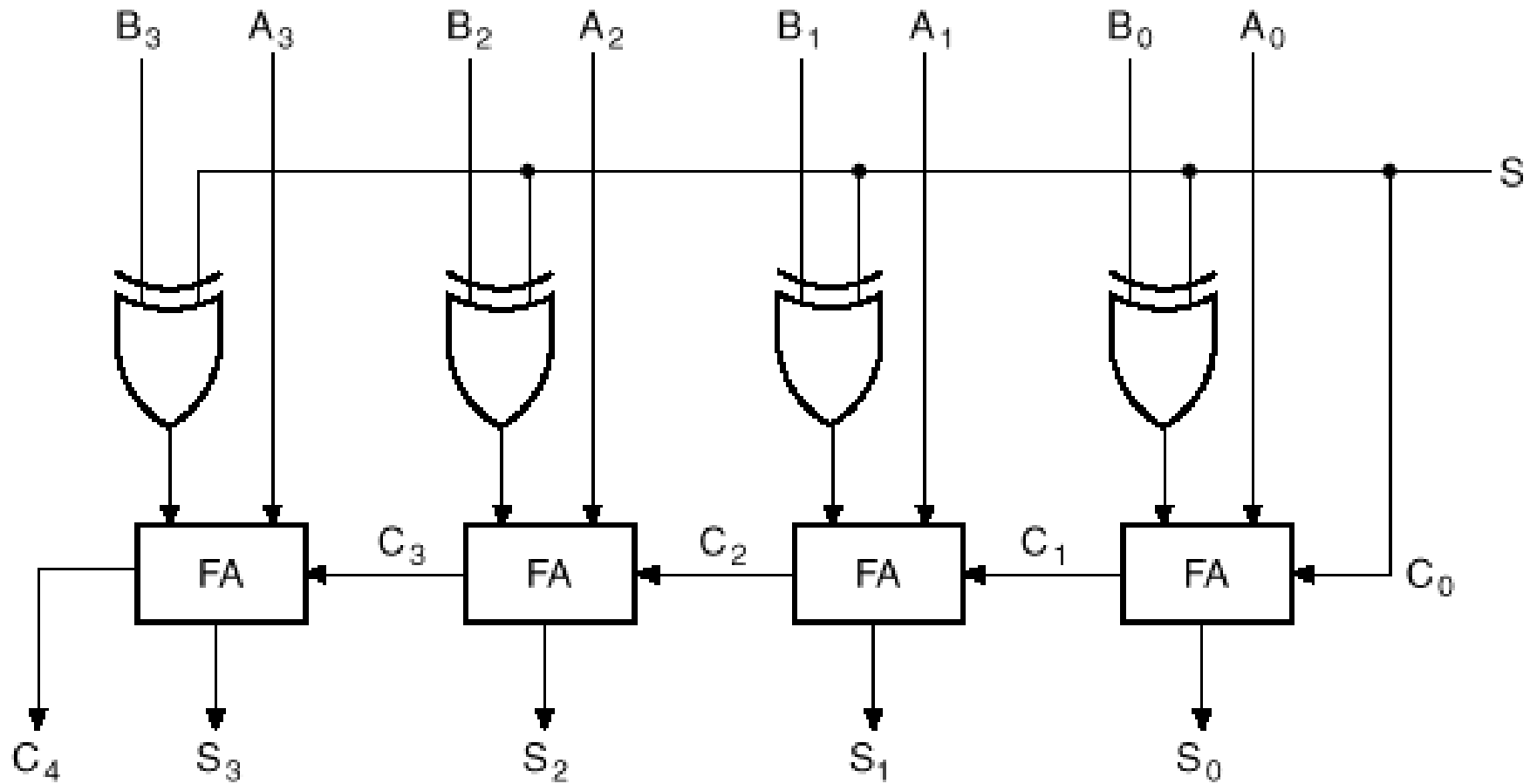

Overflow in two's complement addition

° **Definition:** When two values of the same signs are added:

 - Result won't fit in the number of bits provided
- Result has the opposite sign.



Assumes an N-bit adder, with bit N-1 the MSB

Addition cases and overflow

00	01	11	10	00	11
0010	0011	1110	1101	0010	1110
0011	0110	1101	1010	1100	0100
-----	-----	-----	-----	-----	-----
0101	1001	1011	0111	1110	0010
2	3	-2	-3	2	-2
3	6	-3	-6	-4	4
5	-7	-5	7	-2	2
	OFL		OFL		

Summary

- **Addition and subtraction are fundamental to computer systems**
- **Key – create a single bit adder/subtractor**
 - Chain the single-bit hardware together to create bigger designs
- **The approach is call *ripple-carry* addition**
 - Can be slow for large designs
- **Overflow is an important issue for computers**
 - Processors often have hardware to detect overflow
- **Next time: encoders/decoder.**