

Encoders and Decoders

Overview

◦ Binary decoders

- Converts an n -bit code to a single active output
- Can be developed using AND/OR gates
- Can be used to implement logic circuits.


◦ Binary encoders

- Converts one of 2^n inputs to an n -bit output
- Useful for compressing data
- Can be developed using AND/OR gates

◦ Both encoders and decoders are extensively used in digital systems

Binary Decoder

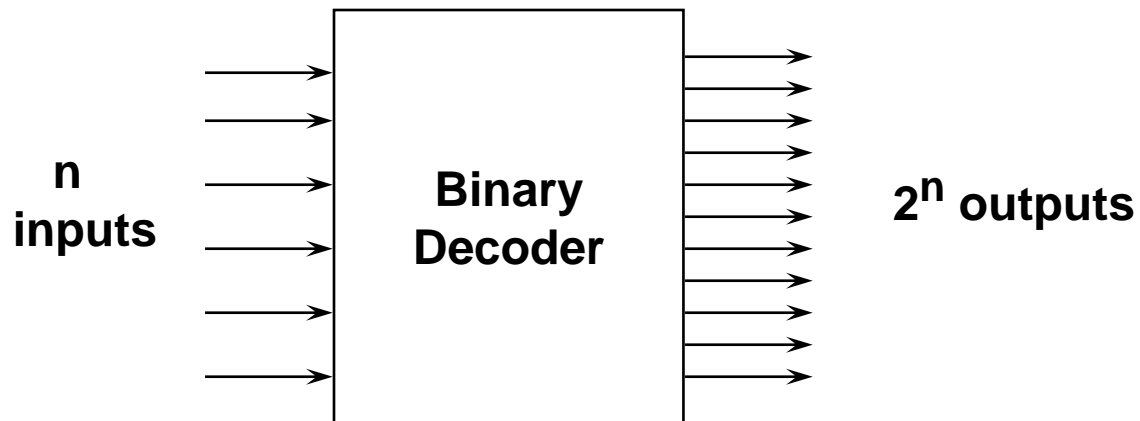- **Black box with n input lines and 2^n output lines**
- **Only one output is a 1 for any given input**





2-to-4 Binary Decoder

Truth Table:

X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

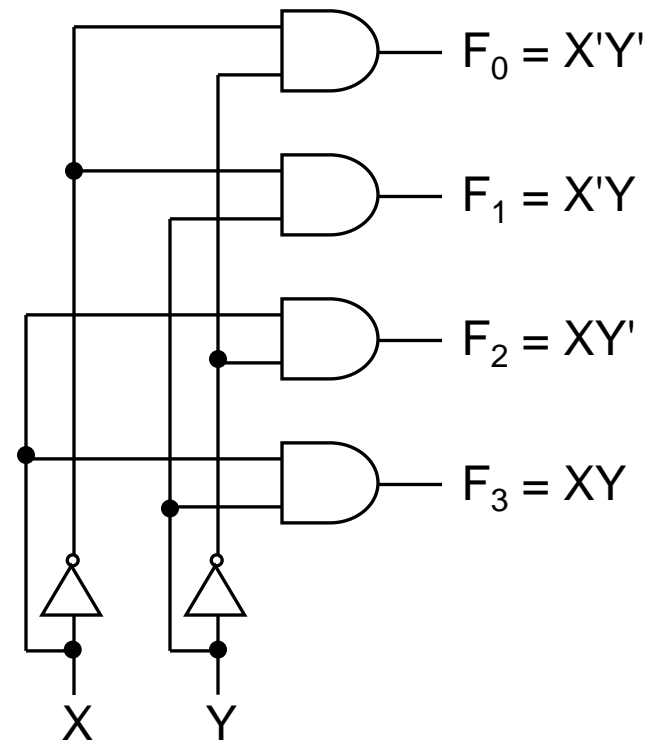
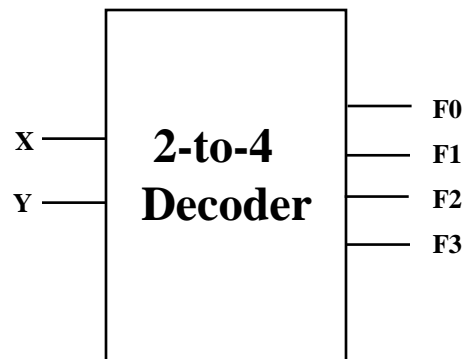
- From truth table, circuit for 2x4 decoder is:
- Note: Each output is a 2-variable minterm ($X'Y'$, $X'Y$, XY' or XY)



3-to-8 Binary Decoder

Truth Table:

x	y	z	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

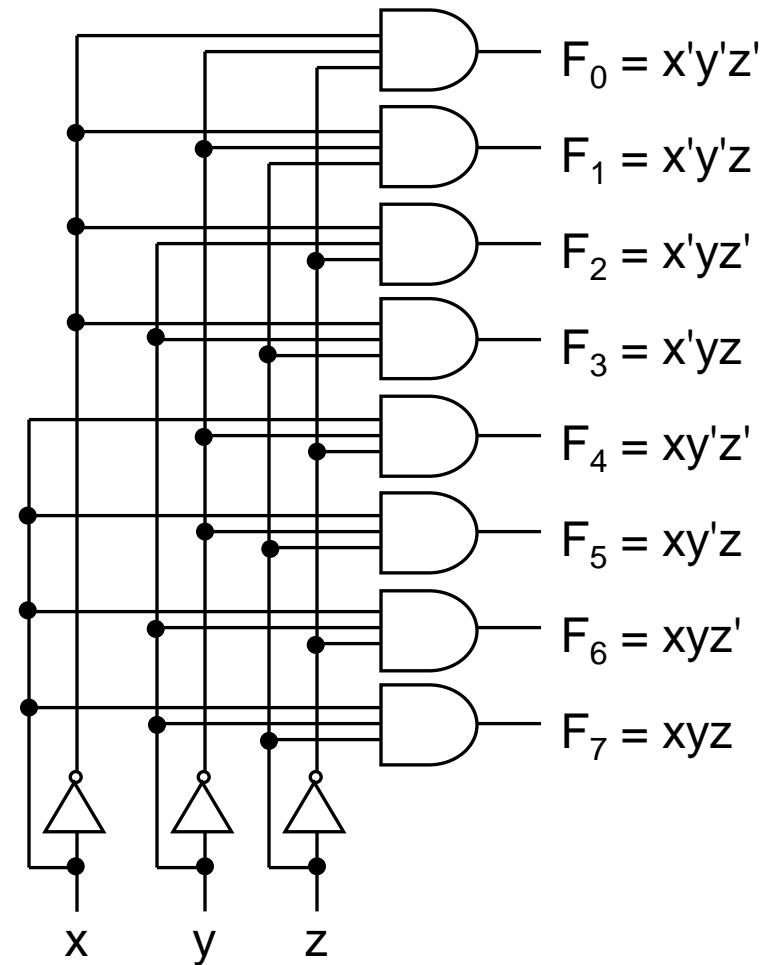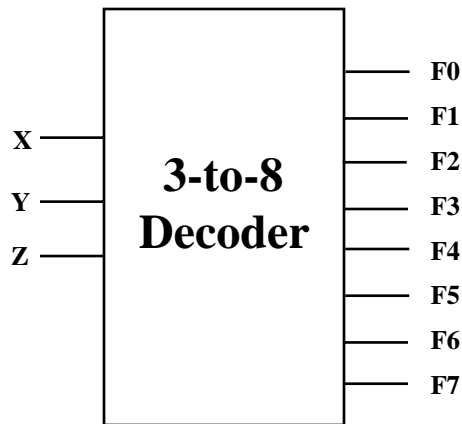

Implementing Functions Using Decoders

- **Any n -variable logic function can be implemented using a single n -to- 2^n decoder to generate the minterms**
 - OR gate forms the sum.
 - The output lines of the decoder corresponding to the minterms of the function are used as inputs to the or gate.
- **Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder with m OR gates.**
- **Suitable when a circuit has many outputs, and each output function is expressed with few minterms.**


Implementing Functions Using Decoders

◦ Example: Full adder

$$S(x, y, z) = \Sigma (1,2,4,7)$$

$$C(x, y, z) = \Sigma (3,5,6,7)$$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

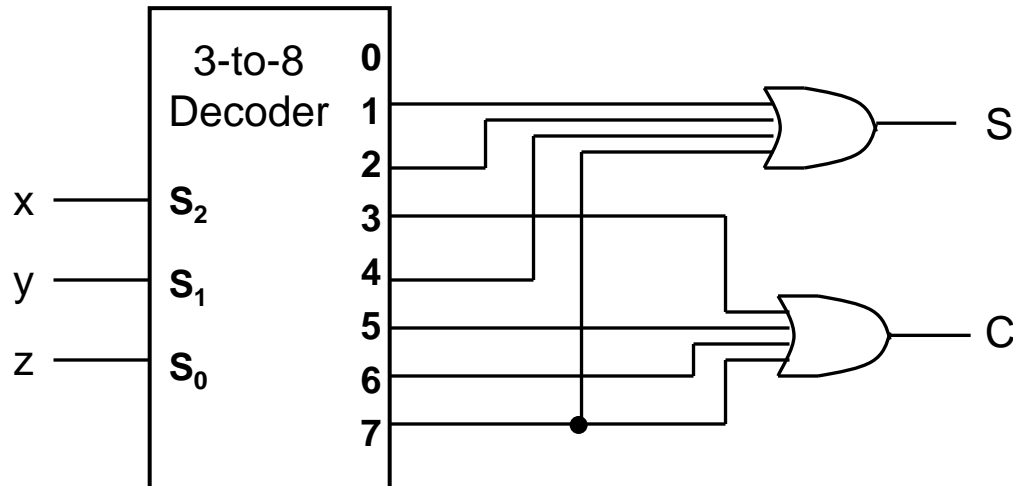


Building a Binary Decoder with NAND Gates

- Start with a 2-bit decoder
 - Add an enable signal (E)

Note: use of NANDs

only one 0 active!

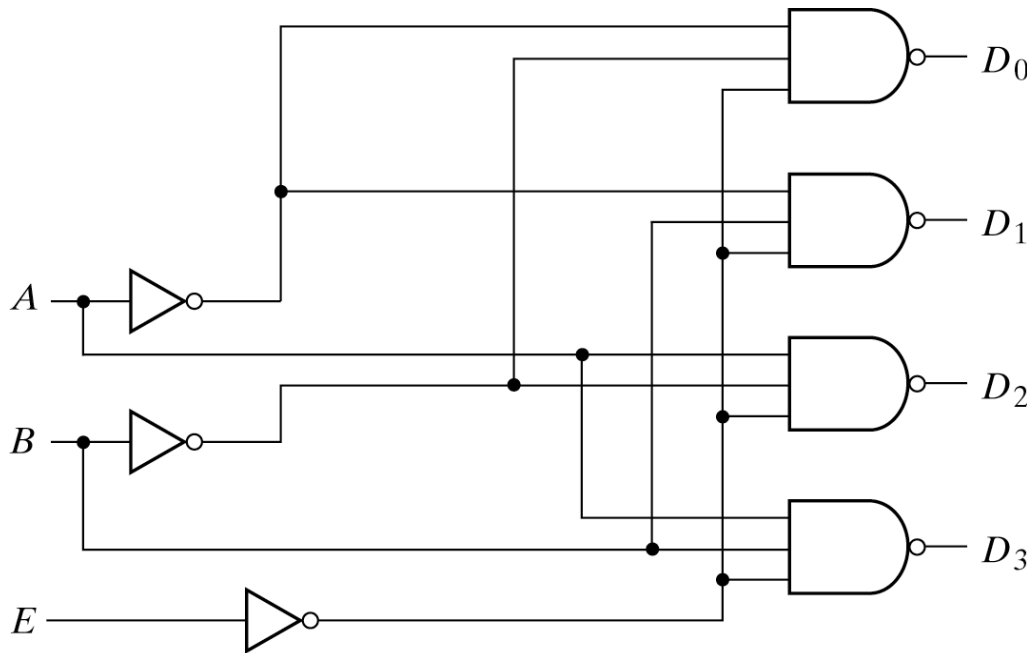

(a) Logic diagram

if E = 0

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

Use two 3 to 8 decoders to make 4 to 16 decoder

- ° Enable can also be active high
- ° In this example, only one decoder can be active at a time.
- ° **x, y, z** effectively select output line for **w**

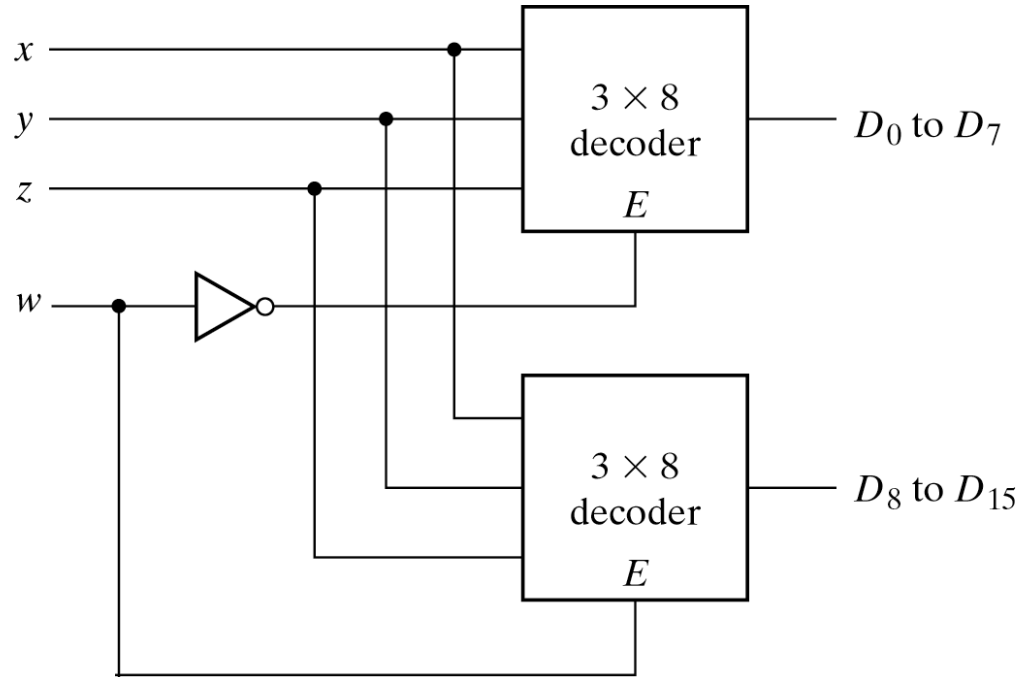



Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders

Encoders

- If the a decoder's output code has fewer bits than the input code, the device is usually called an encoder.

e.g. 2^n -to- n

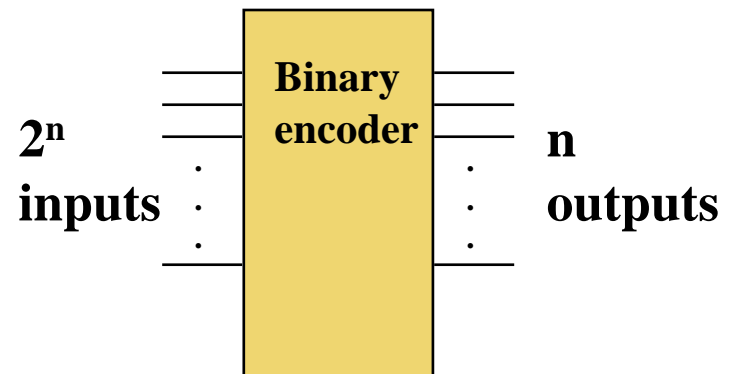
- The simplest encoder is a 2^n -to- n binary encoder
 - One of 2^n inputs = 1
 - Output is an n -bit binary number



8-to-3 Binary Encoder

At any one time, only one input line has a value of 1.

Inputs								Outputs		
I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	y ₂	y ₁	y ₀
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

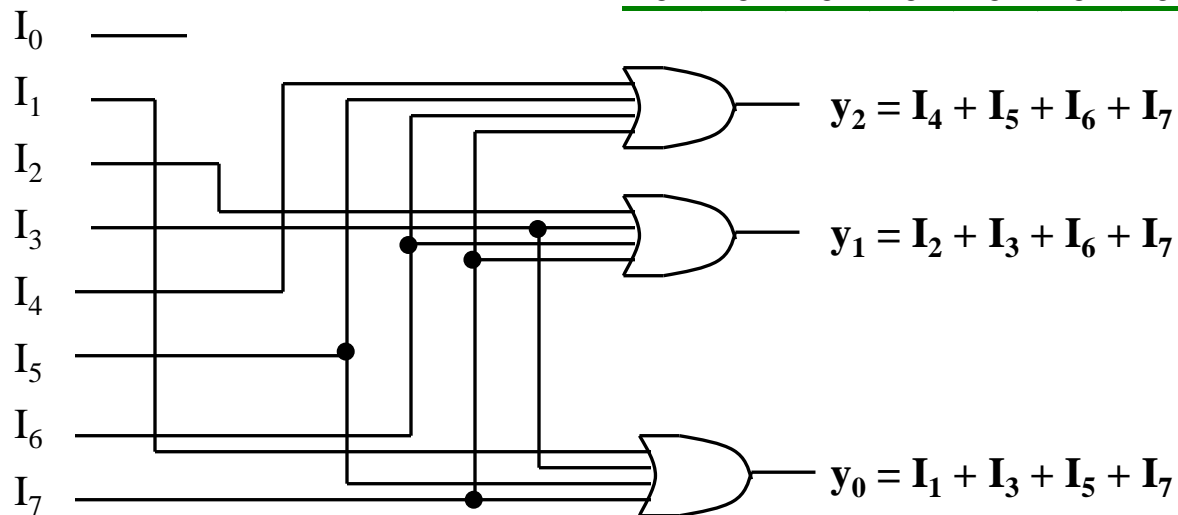

8-to-3 Priority Encoder

- What if more than one input line has a value of 1?
- Ignore “lower priority” inputs.
- **Idle** indicates that no input is a 1.
- Note that polarity of **Idle** is opposite from Table 4-8 in Mano

Inputs								Outputs			
I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	y ₂	y ₁	y ₀	Idle
0	0	0	0	0	0	0	0	x	x	x	1
1	0	0	0	0	0	0	0	0	0	0	0
X	1	0	0	0	0	0	0	0	0	1	0
X	X	1	0	0	0	0	0	0	1	0	0
X	X	X	1	0	0	0	0	0	1	1	0
X	X	X	X	1	0	0	0	1	0	0	0
X	X	X	X	X	1	0	0	1	0	1	0
X	X	X	X	X	X	1	0	1	1	0	0
X	X	X	X	X	X	X	1	1	1	1	0

Summary

- **Decoder allows for generation of a single binary output from an input binary code**
 - For an n -input binary decoder there are 2^n outputs
- **Decoders are widely used in storage devices (e.g. memories)**
 - We will discuss these in a few weeks
- **Encoders all for data compression**
- **Priority encoders rank inputs and encode the highest priority input**
- **Next time: storage elements!**