

Shift Registers

Overview

- **Multiple flip flops can be combined to form a data register**
- **Shift registers allow data to be transported one bit at a time**
- **Registers also allow for parallel transfer**
 - Many bits transferred at the same time
- **Shift registers can be used with adders to build arithmetic units**
- **Remember: most digital hardware can be built from combinational logic (and, or, invert) and flip flops**
 - Basic components of most computers

Register with Parallel Load

- **Register: Group of Flip-Flops**
- **Ex: D Flip-Flops**
- **Holds a Word (Nibble) of Data**
- **Loads in Parallel on Clock Transition**
- **Asynchronous Clear (Reset)**

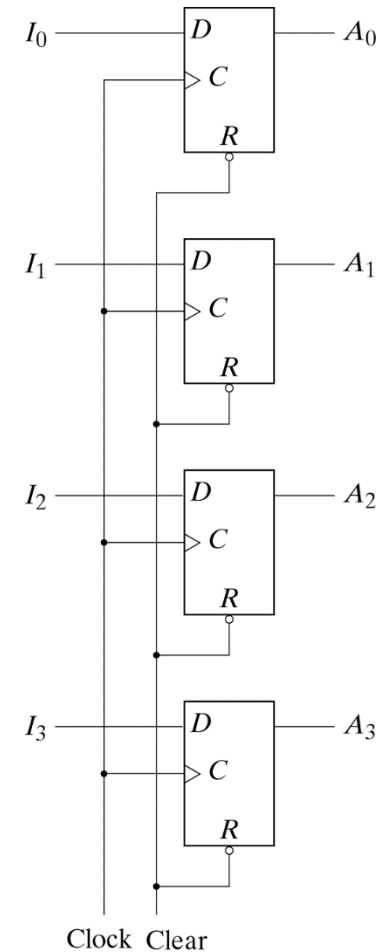


Fig. 6-1 4-Bit Register

Register with Load Control

◦ Load Control = 1

- New data loaded on next positive clock edge

◦ Load Control = 0

- Old data reloaded on next positive clock edge

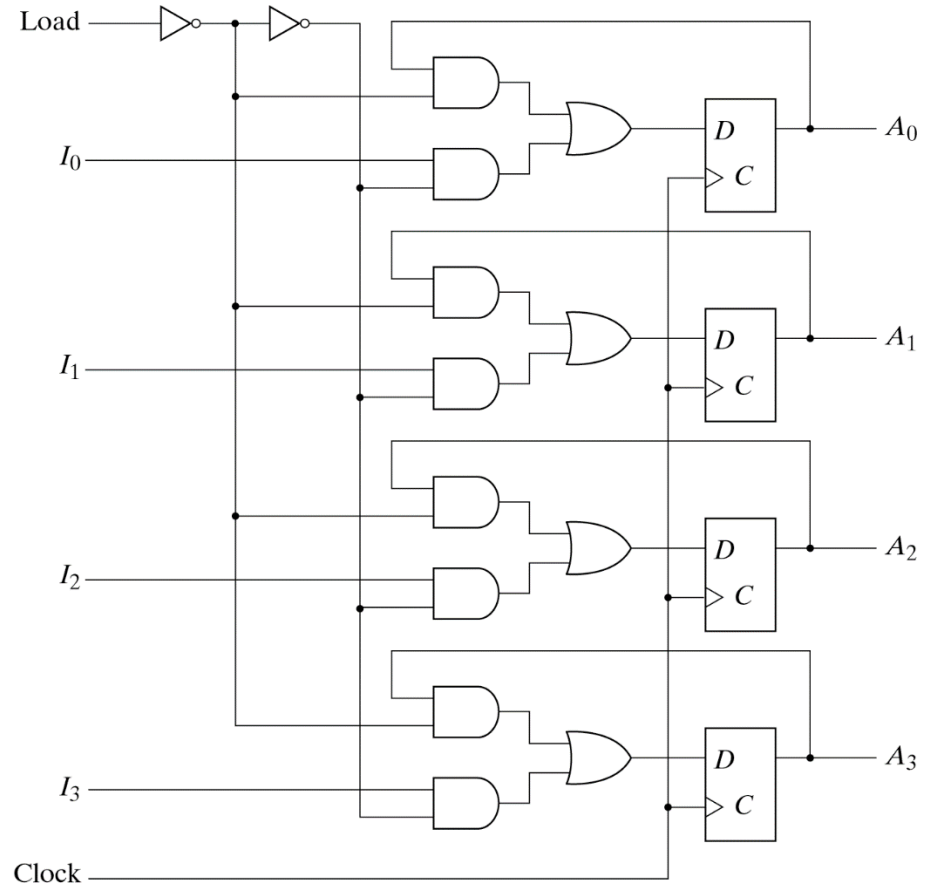


Fig. 6-2 4-Bit Register with Parallel Load

Shift Registers

- Cascade chain of Flip-Flops
- Bits travel on Clock edges
- Serial in – Serial out, can also have parallel load / read


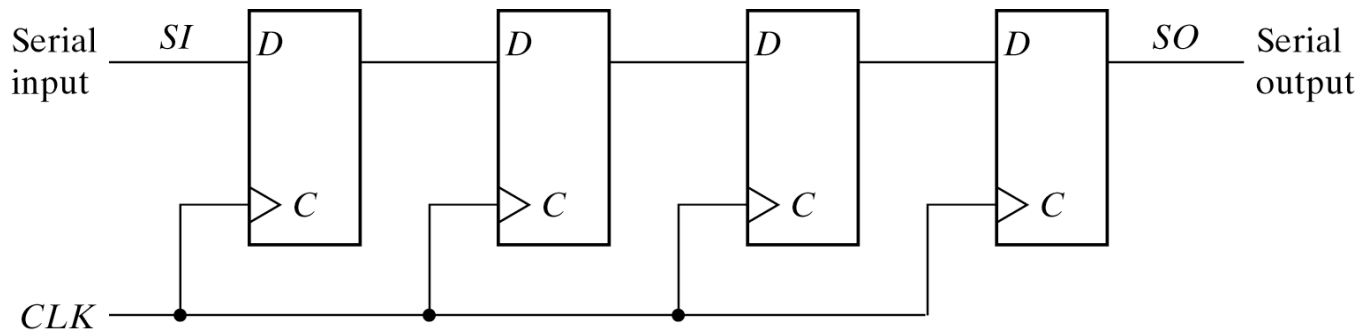


Fig. 6-3 4-Bit Shift Register

Parallel Data Transfer

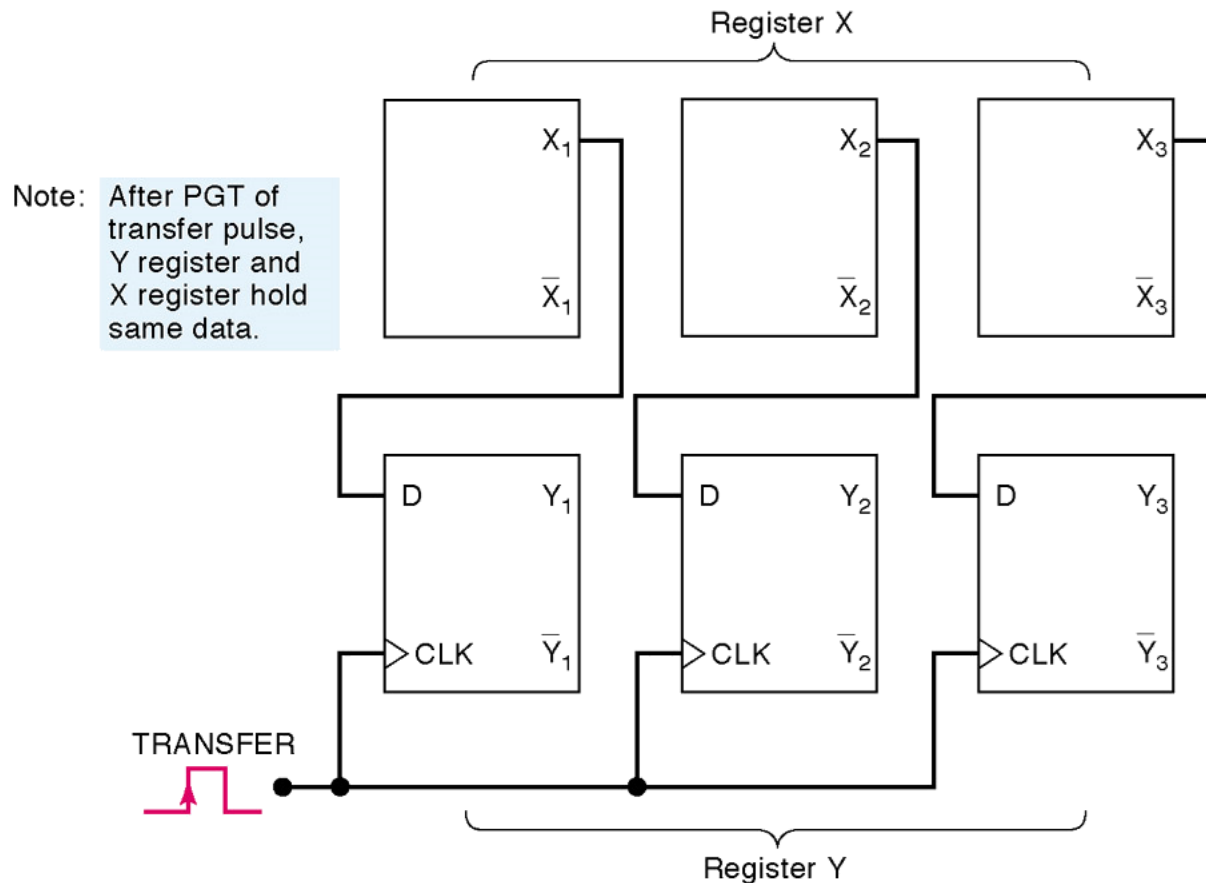
- All data transfers on rising clock edge
- Data clocked into register **Y**



Parallel versus Serial


° Serial communications is defined as

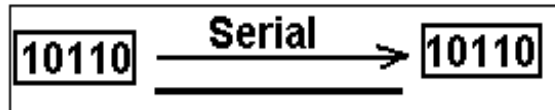- Provides a binary number as a sequence of binary digits, one after another, through one data line.




° Parallel communications

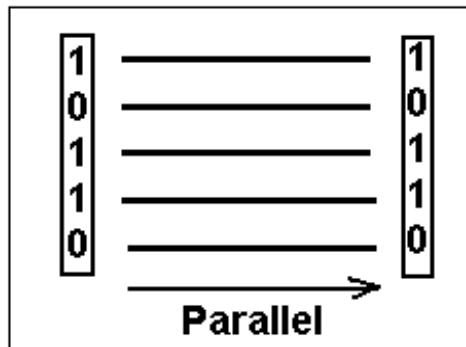- Provides a binary number through multiple data lines at the same time.



Shift register application

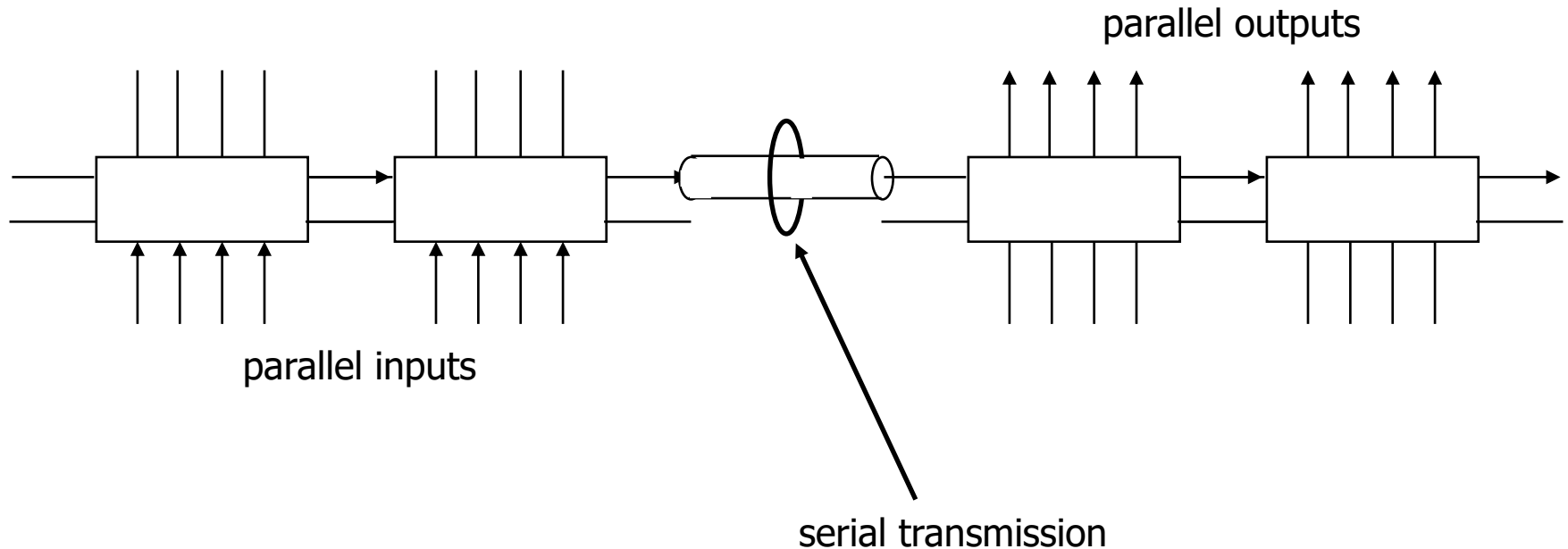° Parallel-to-serial conversion for serial transmission



Serial Transfer

- Data transfer one bit at a time
- Data loopback for register A

Time	Reg A	Reg B
T0	1011	0011
T1	1101	1001
T2	1110	1100
T3	0111	0110
T4	1011	1011


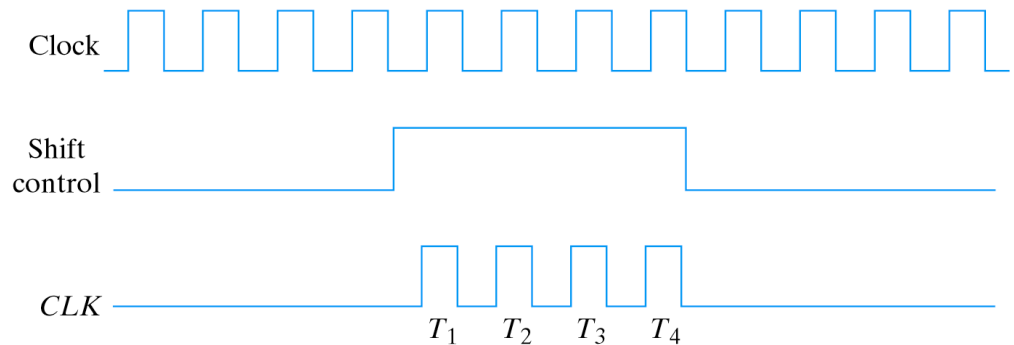
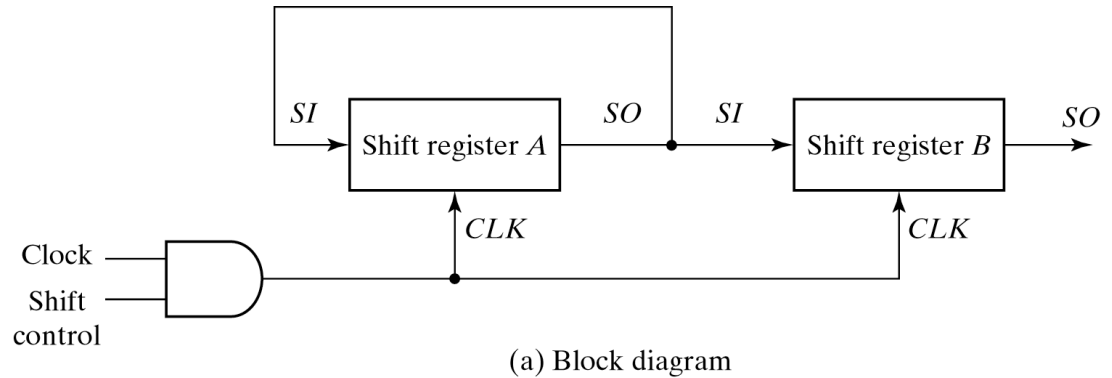


Fig. 6-4 Serial Transfer from Register A to register B

Serial Transfer of Data

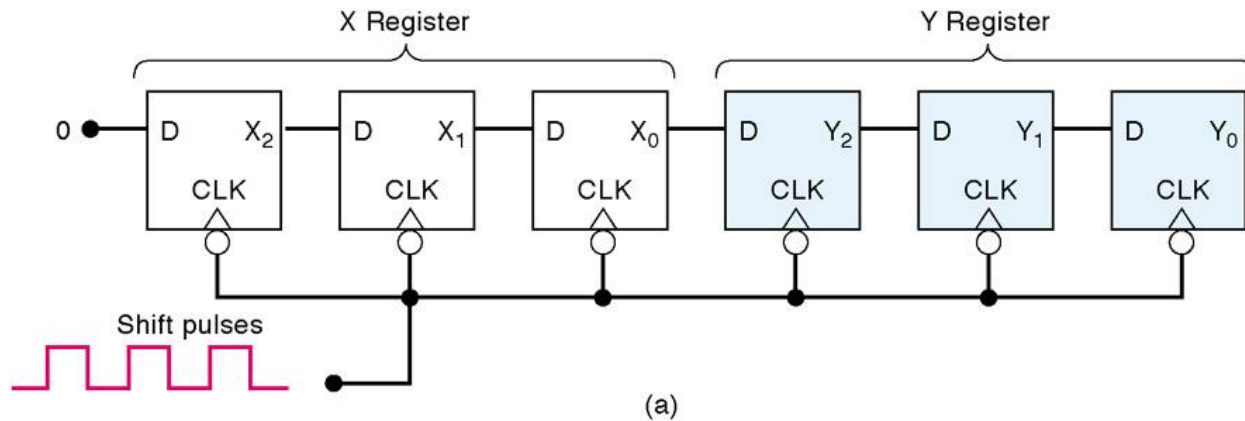- Transfer from register X to register Y (negative clock edges for this example)




X ₂	X ₁	X ₀	Y ₂	Y ₁	Y ₀	
1	0	1	0	0	0	Before pulses applied
0	1	0	1	0	0	After first pulse
0	0	1	0	1	0	After second pulse
0	0	0	1	0	1	After third pulse

(b)

Pattern recognizer

◦ Combinational function of input samples

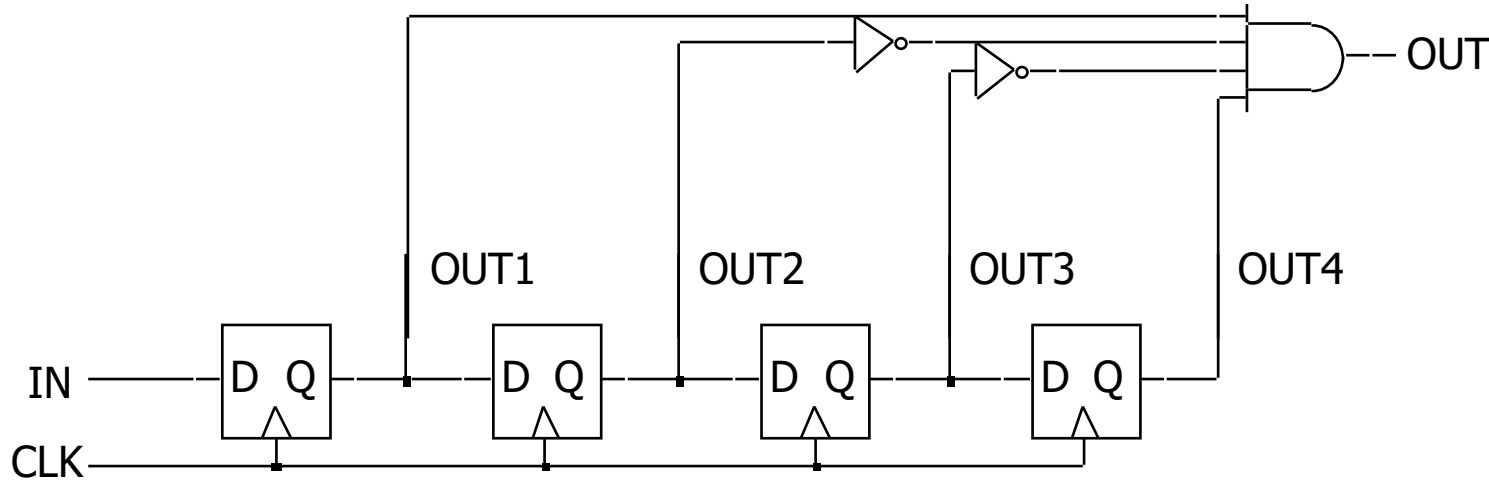- in this case, recognizing the pattern 1001 on the single input signal



Clk	IN	OUT1	OUT2	OUT3	OUT4	OUT
Before						
1	1	0	0	0	0	0
2	0	1	0	0	0	0
3	0	0	1	0	0	0
4	1	0	0	1	0	0
5	0	1	0	0	1	1

Serial Addition (D Flip-Flop)

- **Slower than parallel**
- **Low cost**
- **Share fast hardware on slow data**
- **Good for multiplexed data**

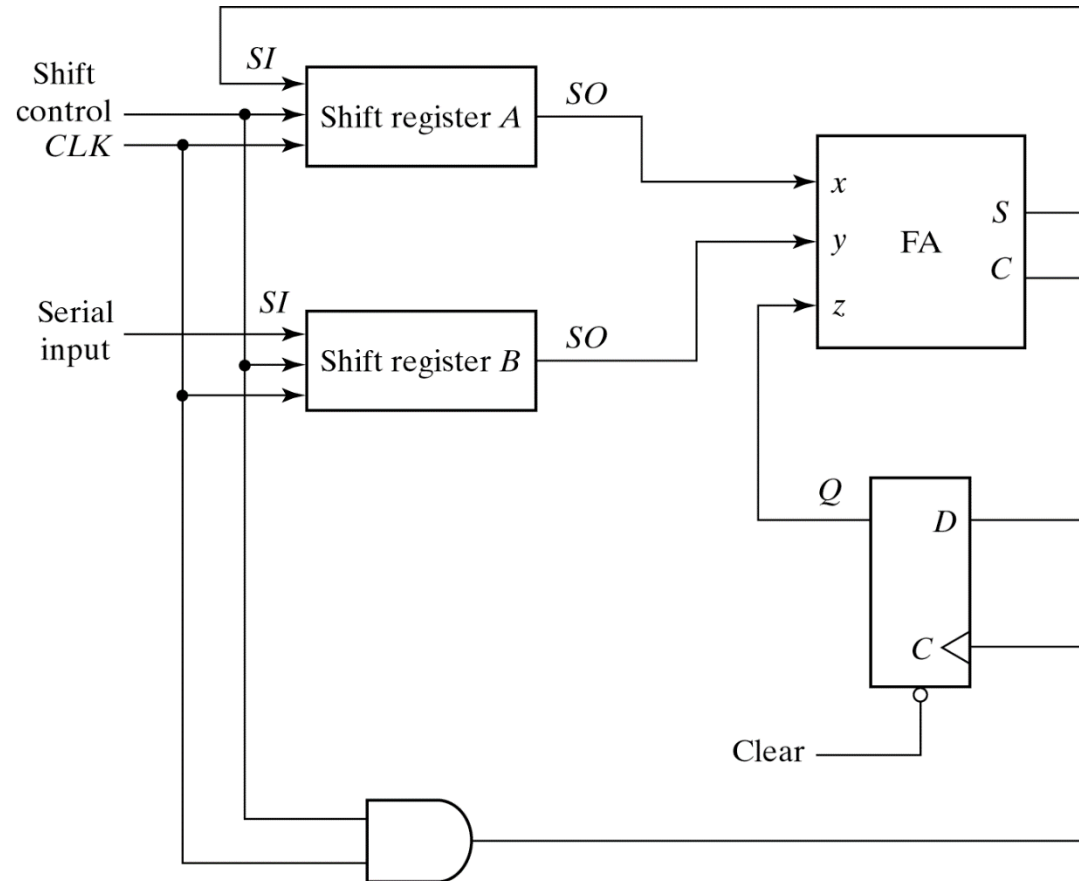


Fig. 6-5 Serial Adder

Serial Addition (D Flip-Flop)

- Only one full adder
- Reused for each bit
- Start with low-order bit addition
- Note that carry (Q) is saved
- Add multiple values.
 - New values placed in **shift register B**

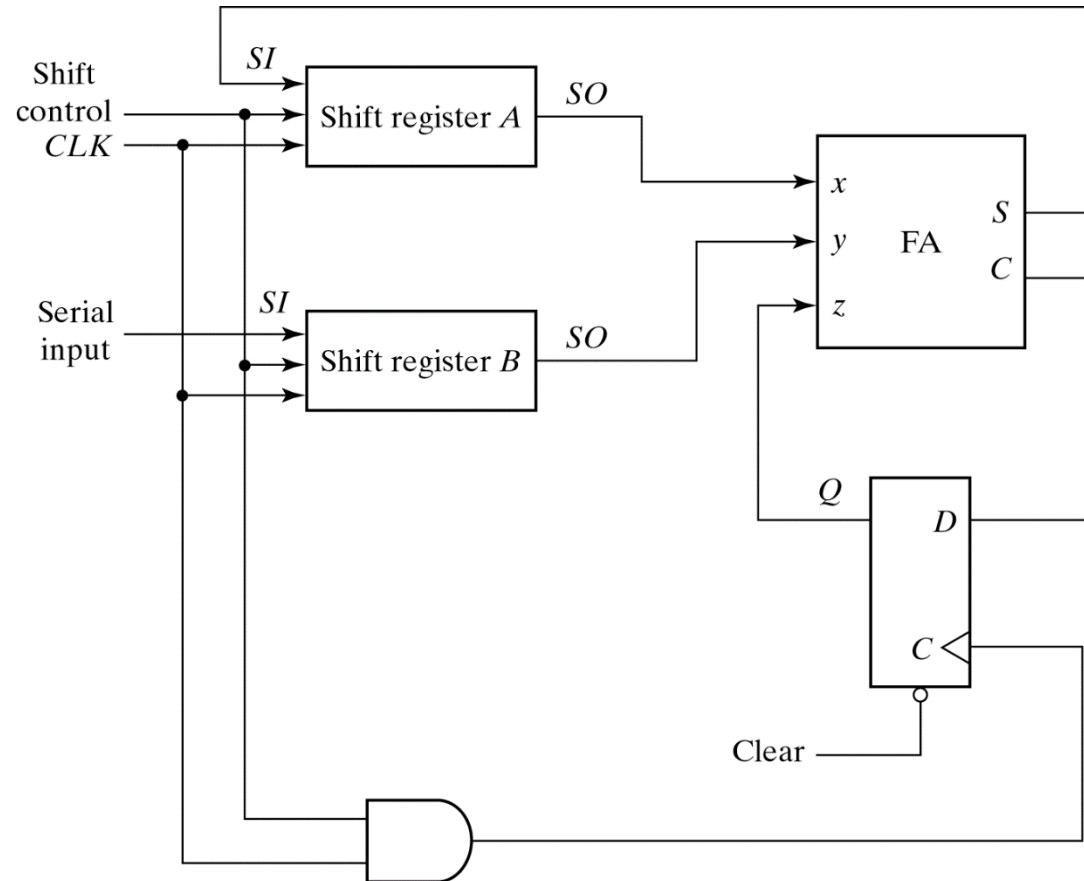


Fig. 6-5 Serial Adder

Serial Addition (D Flip-Flop)

- **Shift control** used to stop addition
- **Generally not a good idea to gate** the clock
- **Shift register** can be arbitrary length
- **FA** can be built from combin. logic

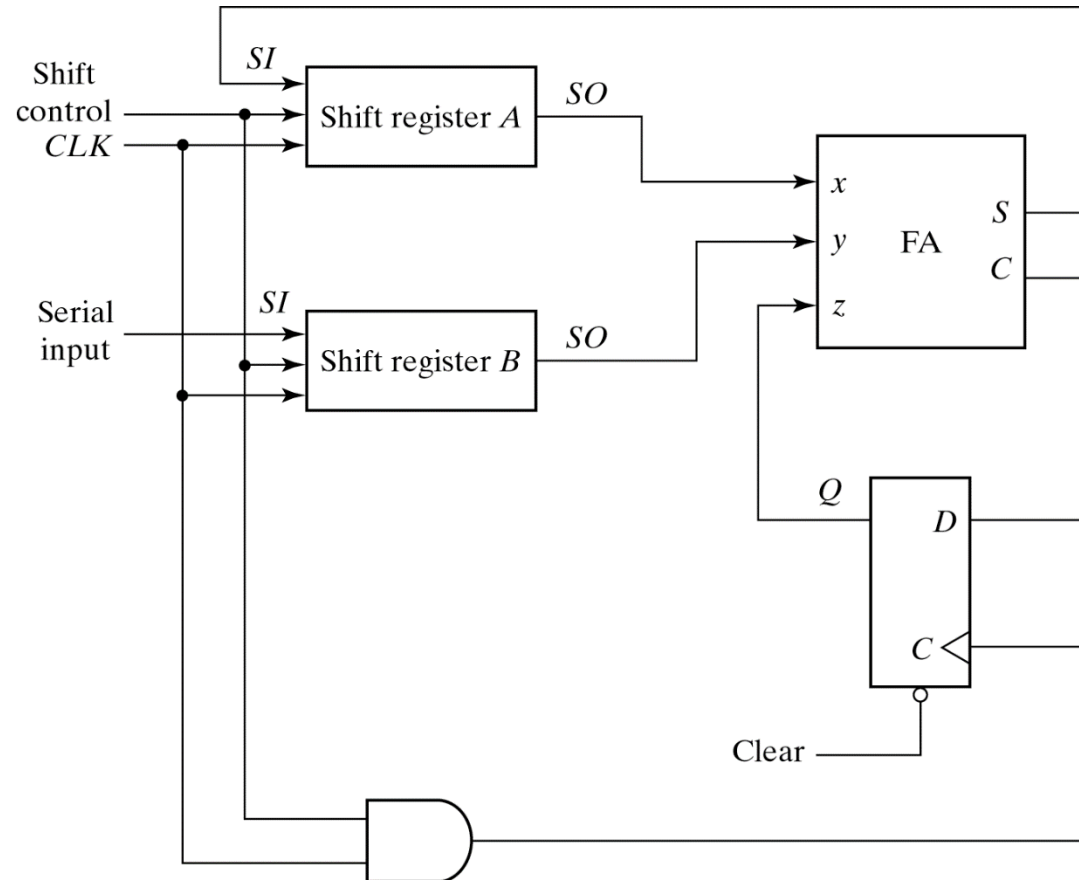


Fig. 6-5 Serial Adder

Universal Shift Register

- Clear
- Clock
- Shift
 - Right
 - Left
- Load
- Read
- Control

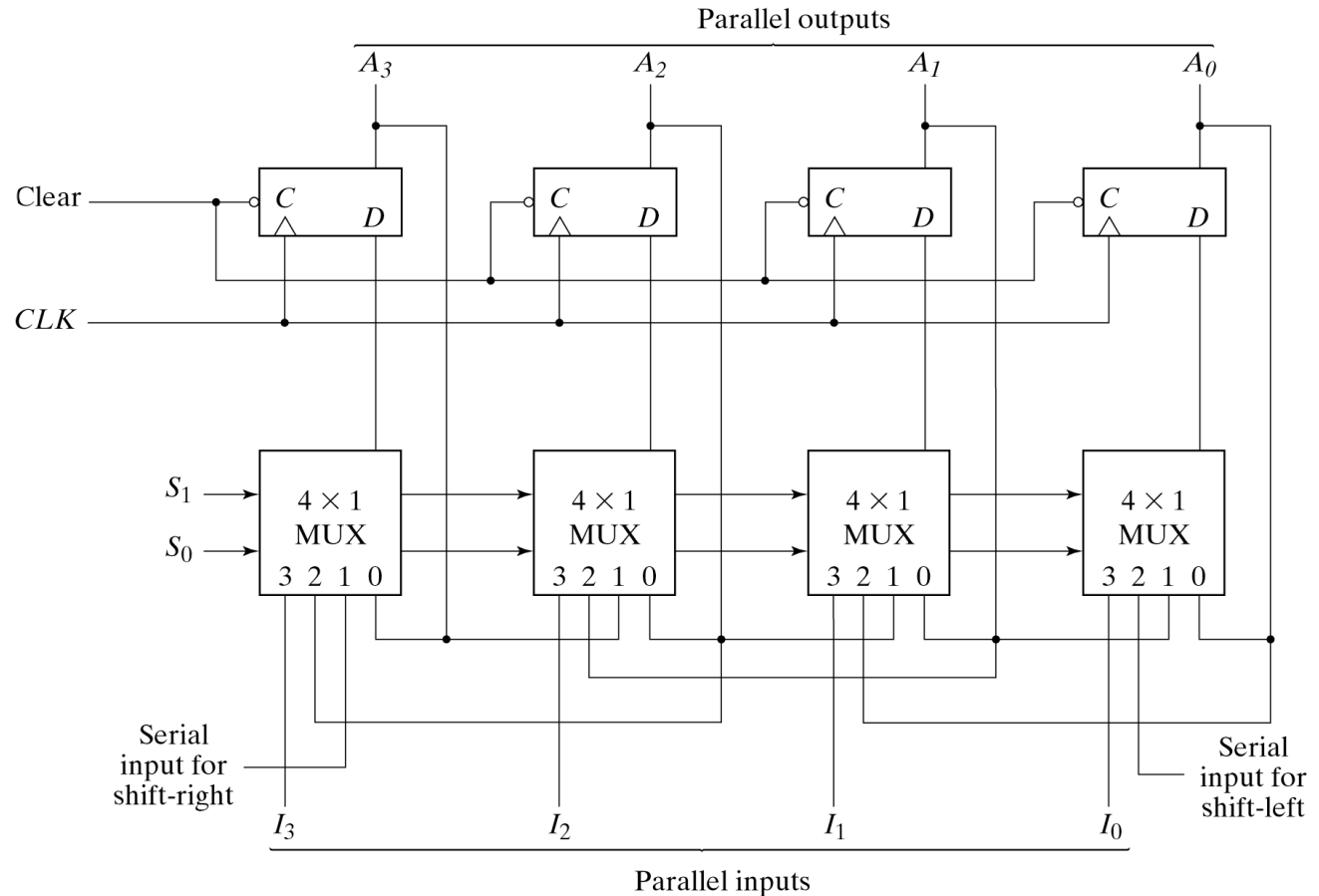


Fig. 6-7 4-Bit Universal Shift Register

Summary

- Shift registers can be combined together to allow for data transfer
- Serial transfer used in modems and computer peripherals (e.g. mouse)
- D flip flops allow for a simple design
 - Data **clocked** in during clock transition (rising or falling edge)
- Serial addition takes less chip area but is slow
- Universal shift register allows for many operations
 - The register is **programmable**.
 - It allows for different operations at different times
- Next time: counters (circuits that count!)