

More Karnaugh Maps and Don't Cares

Overview

- **Karnaugh maps with four inputs**
 - Same basic rules as three input K-maps
- **Understanding prime implicants**
 - Related to minterms
- **Covering all implicants**
- **Using Don't Cares to simplify functions**
 - Don't care outputs are undefined
- **Summarizing Karnaugh maps**

Karnaugh Maps for Four Input Functions

- Represent functions of 4 inputs with 16 minterms
- Use same rules developed for 3-input functions
- Note bracketed sections shown in example.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

(a)

		yz		y	
		00	01	11	10
wx	00	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	01	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		z			

(b)



Fig. 3-8 Four-variable Map

Karnaugh map: 4-variable example

° $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$

$F =$

$$C + A'BD + B'D'$$

  

Solution set can be considered as a coordinate System!

Design examples

	A				
	0	0	0	0	
	1	0	0	0	
	1	1	0	1	D
C	1	1	0	0	
	B				

K-map for LT

	A				
	1	0	0	0	
	0	1	0	0	
	0	0	1	0	D
C	0	0	0	1	
	B				

K-map for EQ

	A				
	0	1	1	1	
	0	0	1	1	D
	0	0	0	0	
C	0	0	1	0	
	B				

K-map for GT


$$LT = A' B' D + A' C + B' C D$$

$$EQ = A' B' C' D' + A' B C' D + A B C D + A B' C D'$$

$$GT = B C' D' + A C' + A B D'$$

Can you draw the truth table for these examples?

Physical Implementation

 

- Step 1: Truth table
- Step 2: K-map
- Step 3: Minimized sum-of-products
- Step 4: Physical implementation with gates

A				D
1	0	0	0	
0	1	0	0	
0	0	1	0	
C	0	0	0	1
	0	0	0	1
B				D

K-map for EQ

Karnaugh Maps

- Four variable maps.

		CD			
		00	01	11	10
AB	00	0	0	0	1
	01	1	1	0	1
	11	1	1	1	1
	10	1	0	1	1

$$F = A'BC' + A'CD' + ABC \\ + AB'C'D' + ABC' + AB'C$$

$$F = BC' + CD' + AC + AD'$$

- Need to make sure all 1's are covered
- Try to minimize total product terms.
- Design could be implemented using NANDs and NORs

Karnaugh maps: Don't cares

- In some cases, outputs are undefined
- We “don't care” if the logic produces a 0 or a 1
- This knowledge can be used to simplify functions.

		A			
		00	01	11	10
C	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0

- Treat X's like either 1's or 0's
- Very useful
- OK to leave some X's uncovered

Karnaugh maps: Don't cares

◦ $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$

- without don't cares

- $f =$

$$A'D + C'D$$

		<u>A</u>			
		AB			
		00	01	11	10
CD	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0
		<u>B</u>			
		D			
		C			

A	B	C	D	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	X
1	1	0	1	X
1	1	1	0	0
1	1	1	1	0

Don't Care Conditions

- In some situations, we don't care about the value of a function for certain combinations of the variables.
 - these combinations may be impossible in certain contexts
 - or the value of the function may not matter in when the combinations occur
- In such situations we say the function is *incompletely specified* and there are multiple (completely specified) logic functions that can be used in the design.
 - so we can select a function that gives the simplest circuit
- When constructing the terms in the simplification procedure, we can choose to either cover or not cover the don't care conditions.

Map Simplification with Don't Cares

$AB \backslash CD$		CD			
		00	01	11	10
00	00	0	1	0	0
01	01	x	x	x	1
11	11	1	1	1	x
10	10	x	0	1	1

$$F=A'C'D+B+AC$$

◦ **Alternative covering.**

$AB \backslash CD$		CD			
		00	01	11	10
00	00	0	1	0	0
01	01	x	x	x	1
11	11	1	1	1	x
10	10	x	0	1	1

$$F=A'B'C'D+ABC'+BC+AC$$

Karnaugh maps: don't cares (cont'd)

◦ $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

• $f = A'D + B'C'D$

without don't cares

• $f =$

with don't cares

$A'D + C'D$

				A	
		0	0	X	0
		1	1	X	1
		1	1	0	0
		0	X	0	0
		B			
C					
		D			

by using don't care as a "1"
a 2-cube can be formed
rather than a 1-cube to cover
this node

don't cares can be treated as
1s or 0s

depending on which is more
advantageous

Definition of terms for two-level simplification

◦ Implicant

- Single product term of the **ON-set** (terms that create a logic 1)

◦ Prime implicant

- Implicant that can't be combined with another to form an implicant with fewer literals.

◦ Essential prime implicant

- Prime implicant is essential if it alone covers a minterm in the K-map
- Remember that all squares marked with 1 must be covered

◦ Objective:

- Grow implicant into prime implicants (minimize literals per term)
- Cover the K-map with as few prime implicants as possible (minimize number of product terms)

Examples to illustrate terms

				A
	0	X	1	0
	1	1	1	0
C	1	0	1	1
	0	0	1	1
				B

6 prime implicants:

$A'B'D$, BC' , AC , $A'C'D$, AB , $B'CD$

essential

minimum cover: $AC + BC' + A'B'D$

5 prime implicants:

BD , ABC' , ACD , $A'BC$, $A'C'D$

essential

minimum cover: 4 essential implicants


				A
	0	0	1	0
	1	1	1	0
	0	1	1	1
C	0	1	0	0
				B

Prime Implicants

Any single 1 or group of 1s in the Karnaugh map of a function F is an implicant of F .

A product term is called a prime implicant of F if it cannot be combined with another term to eliminate a variable.

Example:

 

If a function F is represented by this Karnaugh Map. Which of the following terms are implicants of F , and which ones are prime implicants of F ?

- (a) $AC'D'$
- (b) BD
- (c) $A'B'C'D'$
- (d) AC'
- (e) $B'C'D'$


Implicants:
(a),(c),(d),(e)

Prime Implicants:
(d),(e)


Essential Prime Implicants

A product term is an essential prime implicant if there is a minterm that is only covered by that prime implicant.

 - The minimal sum-of-products form of F must include all the essential prime implicants of F .



 (a) Essential prime implicants
 BD and $B'D'$



(b) Prime implicants CD , $B'C$,
 AD , and AB'

Fig. 3-11 Simplification Using Prime Implicants

Summary

- **K-maps of four literals considered**
 - **Larger examples exist**
- **Don't care conditions help minimize functions**
 - **Output for don't cares are undefined**
- **Result of minimization is minimal sum-of-products**
- **Result contains prime implicants**
- **Essential prime implicants are required in the implementation**