

# ***State Reduction and Assignment***




# Overview

- Important to minimize the size of digital circuitry
- Analysis of state machines leads to a state table (or diagram)
- In many cases reducing the number of states reduces the number of gates and flops
  - This is not true 100% of the time
- In this course we attempt **state reduction** by examining the state table
- Other, more advanced approaches, possible
- Reducing the number of states generally reduces complexity.

# Finite State Machines

 - Example: Edge Detector


Bits are received one at a time (one per cycle),  
such as: 000111010  $\xrightarrow{\text{time}}$



Design a circuit that asserts  
its output for one cycle when  
the input bit stream changes  
from 0 to 1.

Try two different solutions.


# State Transition Diagram Solution A

 

	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

# Solution A, circuit derivation

	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

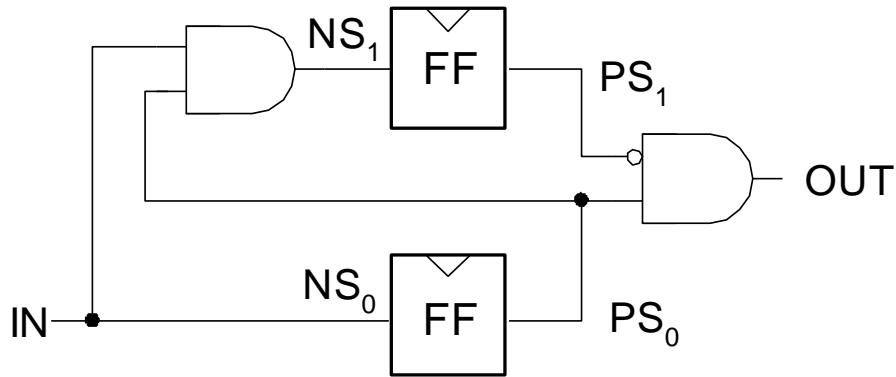

		PS			
		00	01	11	10
IN	0	0	0	0	-
	1	0	1	1	-

$NS_1 = IN \ PS_0$

		PS			
		00	01	11	10
IN	0	0	0	0	-
	1	1	1	1	-


$NS_0 = IN$

		PS			
		00	01	11	10
IN	0	0	1	0	-
	1	0	1	0	-

$OUT = \overline{PS_1} \ PS_0$
 
## Solution B


*Output depends non only on PS but also on input, IN*



Let ZERO=0,  
ONE=1


IN	PS	NS	OUT
0	0	0	0
0	1	0	0
1	0	1	1
1	1	1	0

$NS = IN, OUT = IN \cdot PS'$

 

What's the *intuition* about this solution?

## Edge detector timing diagrams

 


- **Solution A: output follows the clock**
- **Solution B: output changes with input rising edge and is asynchronous wrt the clock.**

# FSM Comparison
 
## ***Solution A***

Moore Machine


- **output function only of PS**
- **maybe more state**
- **synchronous outputs**
  - no glitching
  - one cycle “delay”
  - full cycle of stable output


 
## ***Solution B***

Mealy Machine


- **output function of both PS & input**
- **maybe fewer states**
- **asynchronous outputs**
  - if input glitches, so does output
  - output immediately available
  - output may not be stable long enough to be useful:






# FSM Recap

## Moore Machine

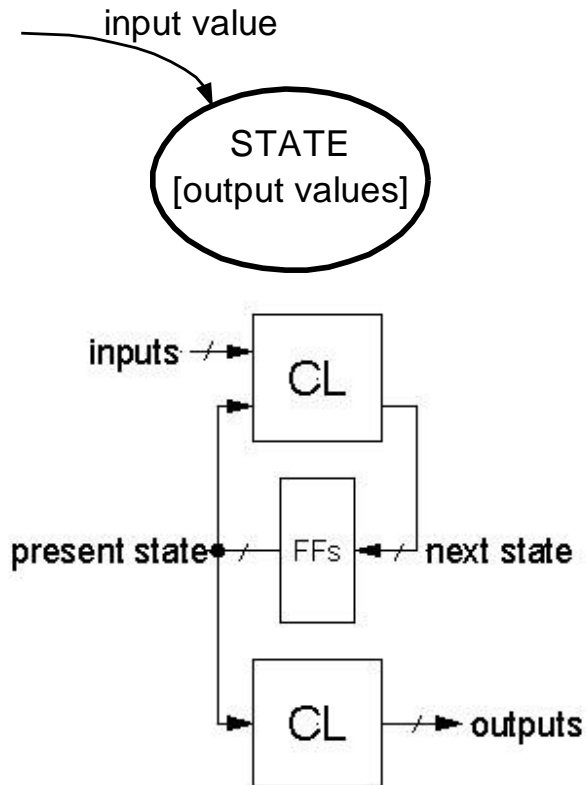

## Mealy Machine

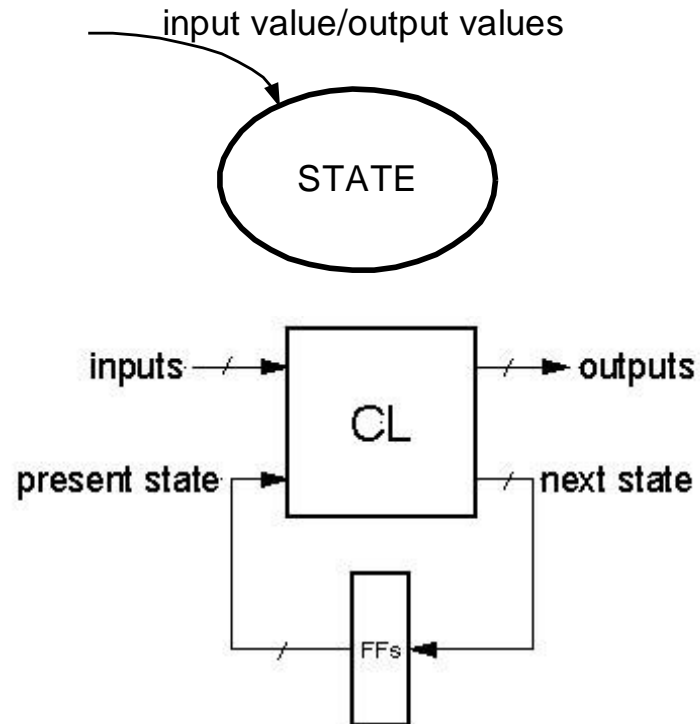

*Both machine types allow one-hot implementations.*

# FSM Optimization

## ◦ State Reduction:


Motivation:

lower cost

- fewer flip-flops in one-hot implementations
- possibly fewer flip-flops in encoded implementations
- more don't cares in next state logic
- fewer gates in next state logic

Simpler to design with extra states then reduce later.

## ◦ Example: Odd parity checker

 

**Moore machine**

# State Reduction

- “Row Matching” is based on the state-transition table:
- If two states
  - have the same output *and* both transition to the same next state
  - *or* both transition to each other
  - *or* both self-loop
  - **then they are equivalent.**
- Combine the equivalent states into a new renamed state.
- Repeat until no more states are combined

State Transition Table

PS	NS		output
	x=0	x=1	
S0	S0	S1	0
S1	S1	S2	1
S2	S2	S1	0



# FSM Optimization

- Merge state S2 into S0
- Eliminate S2
- New state machine shows same I/O behavior


State Transition Table

PS	NS		output
	x=0	x=1	
<u>S0</u>	S0	S1	0
S1	S1	S0	1

- Example: Odd parity checker.

  

# Row Matching Example

 

State Transition Table


PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

# Row Matching Example

PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1


PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

Reduced State Transition Diagram

 
 
# State Reduction

- The “row matching” method is not guaranteed to result in the optimal solution in all cases, because it only looks at pairs of states.
- For example:




- Another (more complicated) method guarantees the optimal solution:
- “Implication table” method:  
**See Mano, chapter 9.**  
**(not responsible for chapter 9 material)**

# Encoding State Variables

- **Option 1: Binary values**
  - 000, 001, 010, 011, 100 ...
- **Option 2: Gray code**
  - 000, 001, 011, 010, 110 ...
- **Option 3: One hot encoding**
  - One bit for every state
  - Only one bit is a one at a given time
  - For a 5-state machine
    - 00001, 00010, 00100, 01000, 10000



# State Transition Diagram Solution B

 

	IN	PS	NS	OUT
ZERO	0	01	01	0
	1	01	10	0
CHANGE	0	10	01	1
	1	10	00	1
ONE	0	00	01	0
	1	00	00	0

- **How does this change the combinational logic?**

# Summary

- Important to create smallest possible FSMs
- This course: use visual inspection method
- Often possible to reduce logic and flip flops
- State encoding is important
  - One-hot coding is popular for flip flop intensive designs.

