


# ***Magnitude Comparators and Multiplexers***

# Overview


- **Discussion of two digital building blocks**
- **Magnitude comparators**
  - Compare two multi-bit binary numbers
  - Create a single bit comparator
  - Use repetitive pattern
- **Multiplexers**
  - Select one out of several bits
  - Some inputs used for selection
  - Also can be used to implement logic
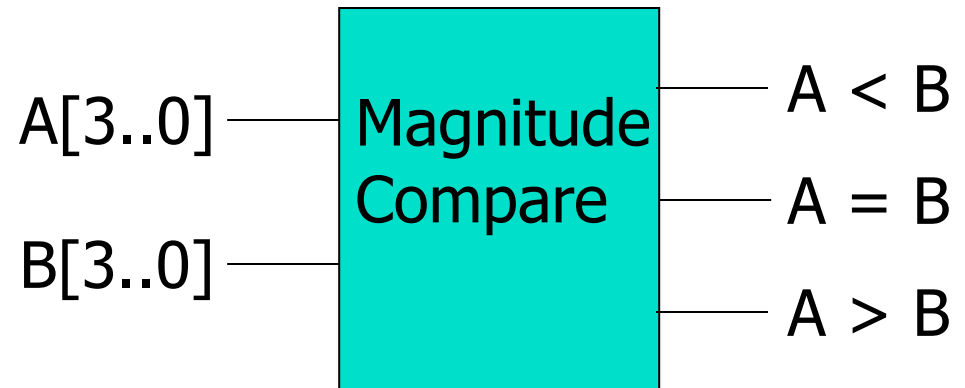
# Magnitude Comparator

- **The comparison of two numbers**
  - outputs:  $A > B$ ,  $A = B$ ,  $A < B$
- **Design Approaches**
  - the truth table
    - $2^{2n}$  entries - too cumbersome for large  $n$
  - use inherent regularity of the problem
    - reduce design efforts
    - reduce human errors



# Magnitude Comparator

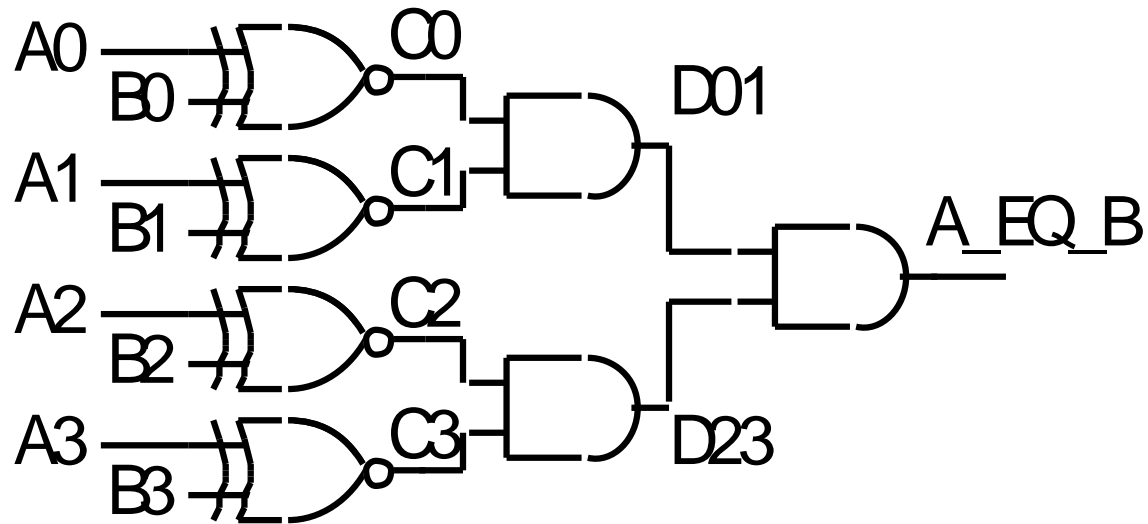


How can we find  $A > B$ ?

How many rows would a truth table have?

$$2^8 = 256$$

# Magnitude Comparator

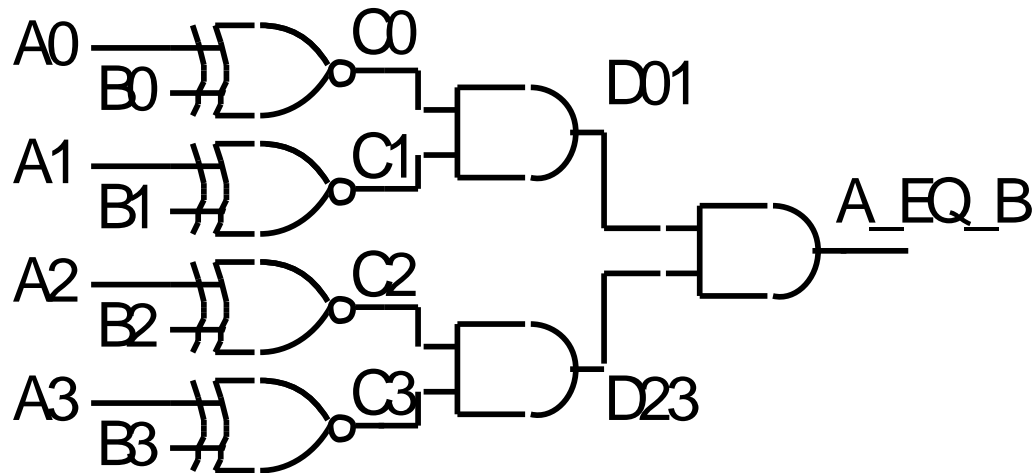

Find  $A > B$

If  $A = 1001$  and  
 $B = 0111$   
is  $A > B$ ?

Why?

Because  $A_3 > B_3$   
i.e.  $A_3 \cdot B_3' = 1$

Therefore, one term in the  
logic equation for  $A > B$  is  
 $A_3 \cdot B_3'$

# Magnitude Comparator

If  $A = 10\textcolor{red}{1}0$  and

$B = 100\textcolor{red}{1}$

is  $A > B$ ?

Why?

$$A > B = A_3 \cdot B_3'$$

$$+ C_3 \cdot A_2 \cdot B_2'$$

$$+ \dots$$

Because  $A_3 = B_3$  and

$A_2 = B_2$  and

$$\textcolor{red}{A_1} > \textcolor{red}{B_1}$$

i.e.  $C_3 = 1$  and  $C_2 = 1$  and

$$A_1 \cdot B_1' = 1$$

Therefore, the next term in the logic equation for  $A > B$  is

$$C_3 \cdot C_2 \cdot A_1 \cdot B_1'$$

# Magnitude Comparison

- **Algorithm -> logic**

- $A = A_3A_2A_1A_0$  ;  $B = B_3B_2B_1B_0$
- $A=B$  if  $A_3=B_3$ ,  $A_2=B_2$ ,  $A_1=B_1$  and  $A_0=B_0$

- **Test each bit:**


- equality:  $x_i = A_iB_i + A_i'B_i'$
- $(A=B) = x_3x_2x_1x_0$

- **More difficult to test less than/greater than**

- $(A>B) = A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$
- $(A<B) = A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$
- Start comparisons from **high-order** bits

- **Implementation**

- $x_i = (A_iB_i' + A_i'B_i)'$

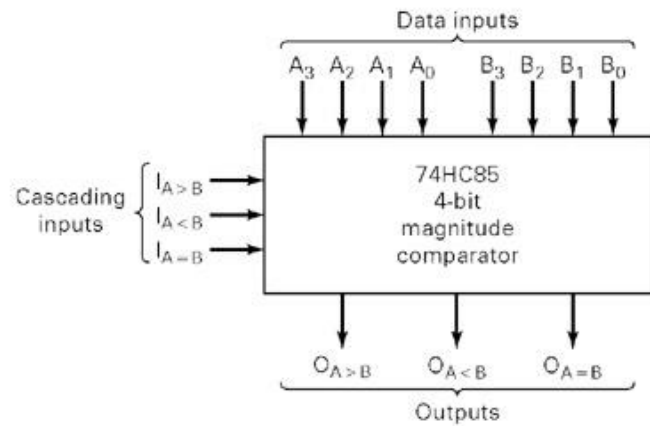

TRUTH TABLE

COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
A <sub>3</sub> , B <sub>3</sub>	A <sub>2</sub> , B <sub>2</sub>	A <sub>1</sub> , B <sub>1</sub>	A <sub>0</sub> , B <sub>0</sub>	I <sub>A&gt;B</sub>	I <sub>A&lt;B</sub>	I <sub>A=B</sub>	O <sub>A&gt;B</sub>	O <sub>A&lt;B</sub>	O <sub>A=B</sub>
A <sub>3</sub> > B <sub>3</sub>	X	X	X	X	X	X	H	L	L
A <sub>3</sub> < B <sub>3</sub>	X	X	X	X	X	X	L	H	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> > B <sub>2</sub>	X	X	X	X	X	H	L	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> < B <sub>2</sub>	X	X	X	X	X	L	H	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> > B <sub>1</sub>	X	X	X	X	H	L	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> < B <sub>1</sub>	X	X	X	X	L	H	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> = B <sub>1</sub>	A <sub>0</sub> > B <sub>0</sub>	X	X	X	H	L	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> = B <sub>1</sub>	A <sub>0</sub> < B <sub>0</sub>	X	X	X	L	H	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> = B <sub>1</sub>	A <sub>0</sub> = B <sub>0</sub>	H	L	L	H	L	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> = B <sub>1</sub>	A <sub>0</sub> = B <sub>0</sub>	L	H	L	L	H	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> = B <sub>1</sub>	A <sub>0</sub> = B <sub>0</sub>	X	X	H	L	L	H
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> = B <sub>1</sub>	A <sub>0</sub> = B <sub>0</sub>	L	L	L	H	H	L
A <sub>3</sub> = B <sub>3</sub>	A <sub>2</sub> = B <sub>2</sub>	A <sub>1</sub> = B <sub>1</sub>	A <sub>0</sub> = B <sub>0</sub>	H	H	L	L	L	L

H = HIGH Voltage Level


L = LOW Voltage Level

X = Immaterial



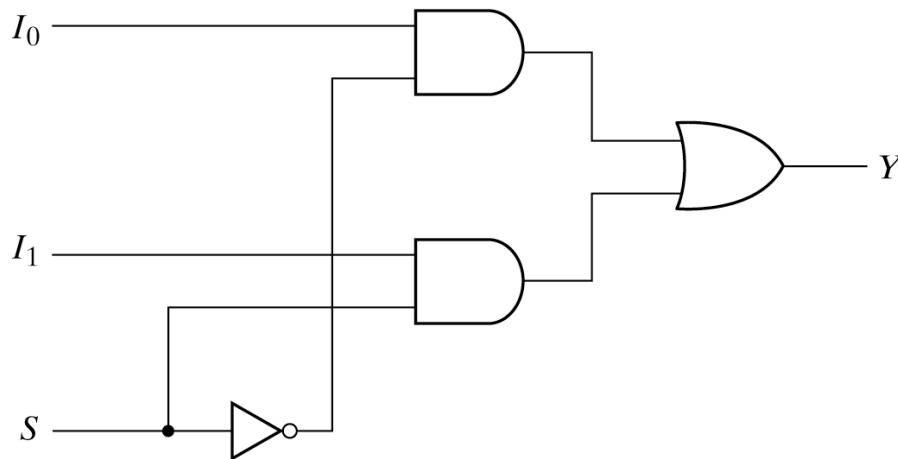
# Multiplexers

- Select an input value with one or more select bits
- Use for transmitting data
- Allows for **conditional** transfer of data
- Sometimes called a **mux**




(a) Logic diagram

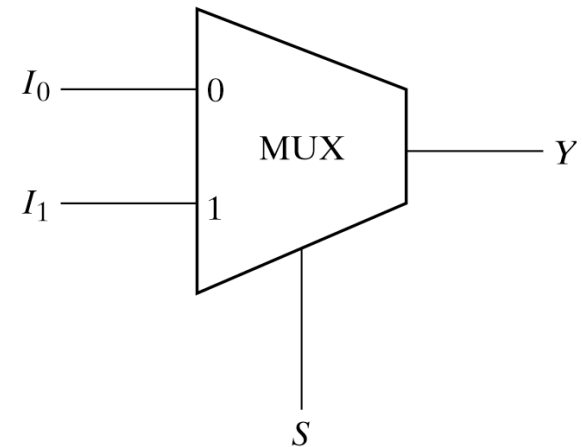


(b) Block diagram

Fig. 4-24 2-to-1-Line Multiplexer

## 4- to- 1- Line Multiplexer

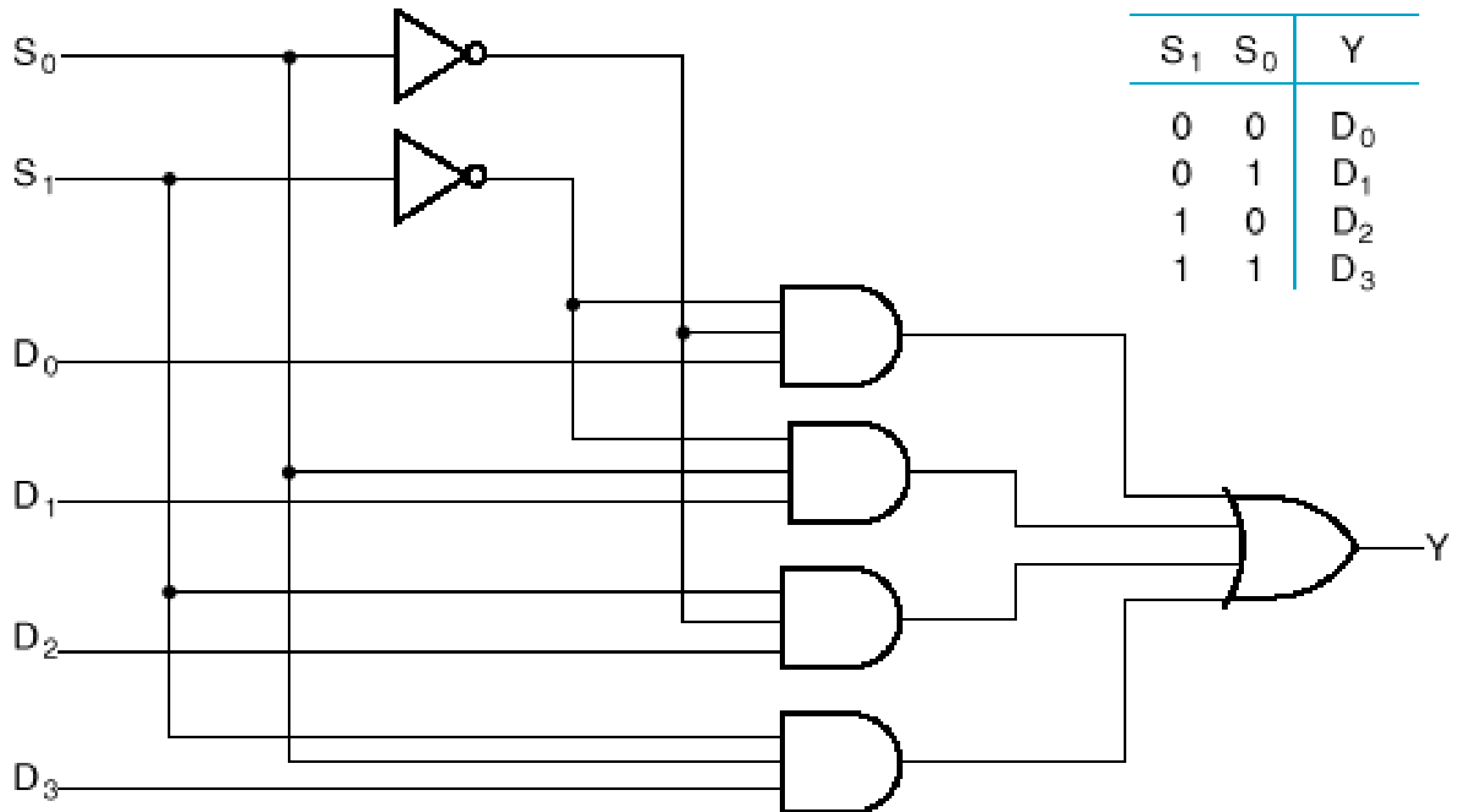

# Quadruple 2-to-1-Line Multiplexer

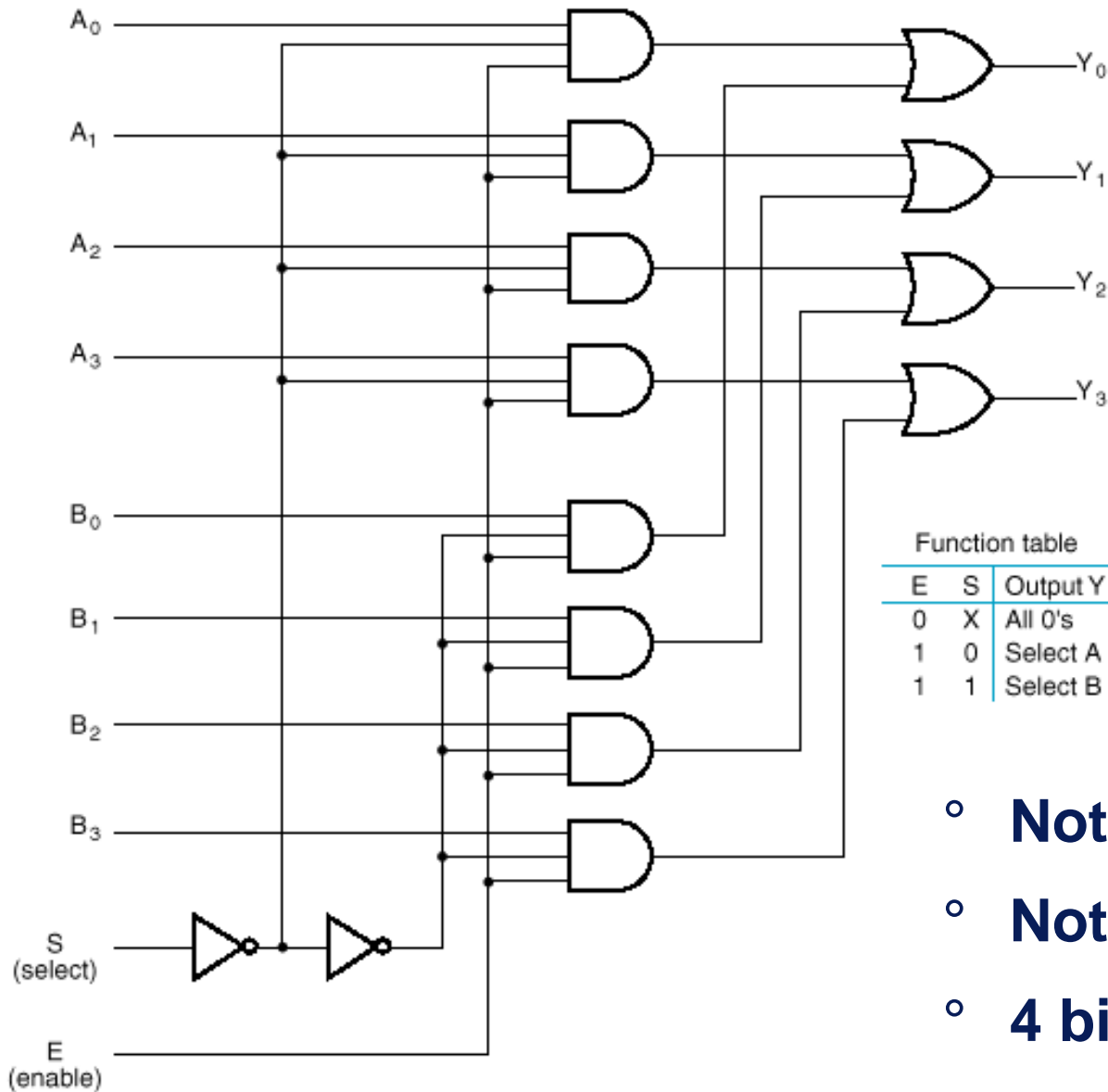


## Multiplexer as combinational modules

- Connect input variables to select inputs of multiplexer ( $n-1$  for  $n$  variables)
- Set data inputs to multiplexer equal to values of function for corresponding assignment of select variables
- Using a variable at data inputs reduces size of the multiplexer

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a) Truth table

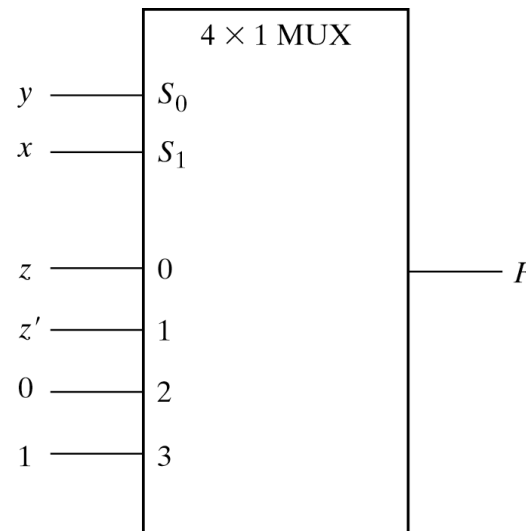


(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

# Implementing a Four- Input Function with a Multiplexer

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

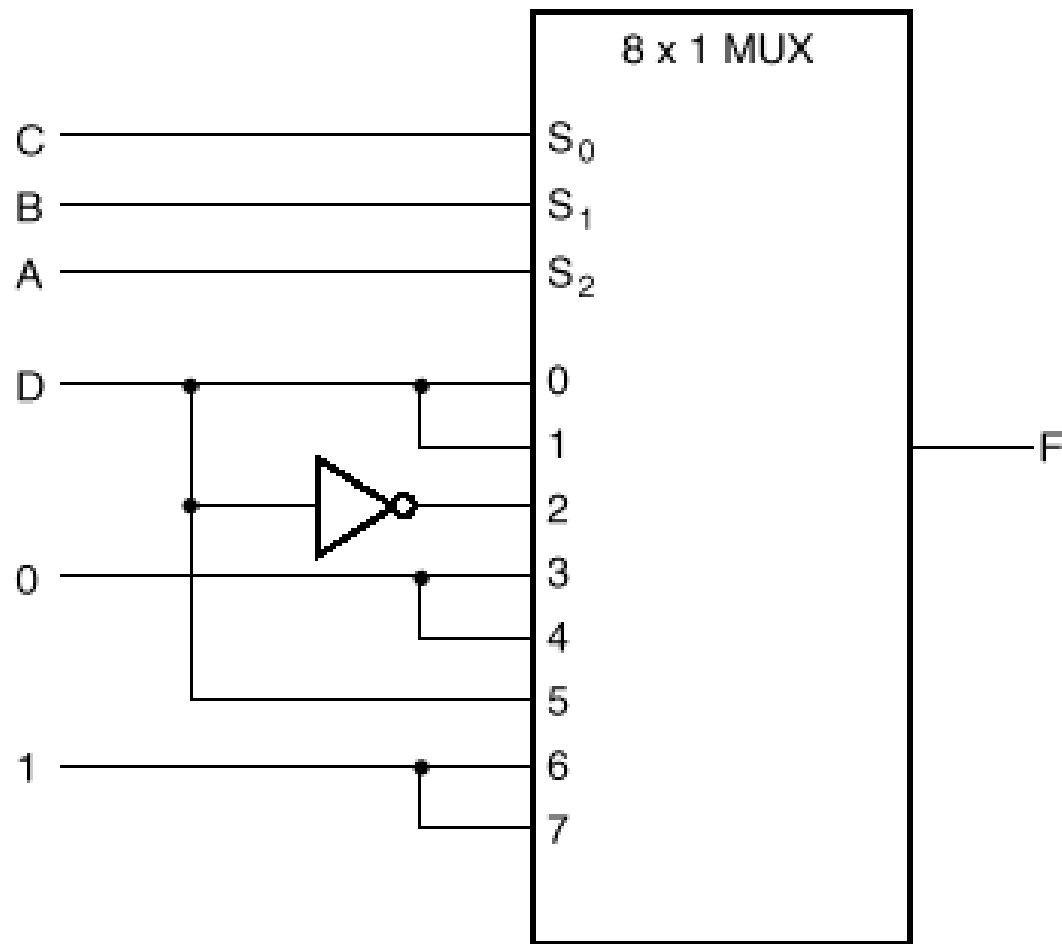

# Typical multiplexer uses


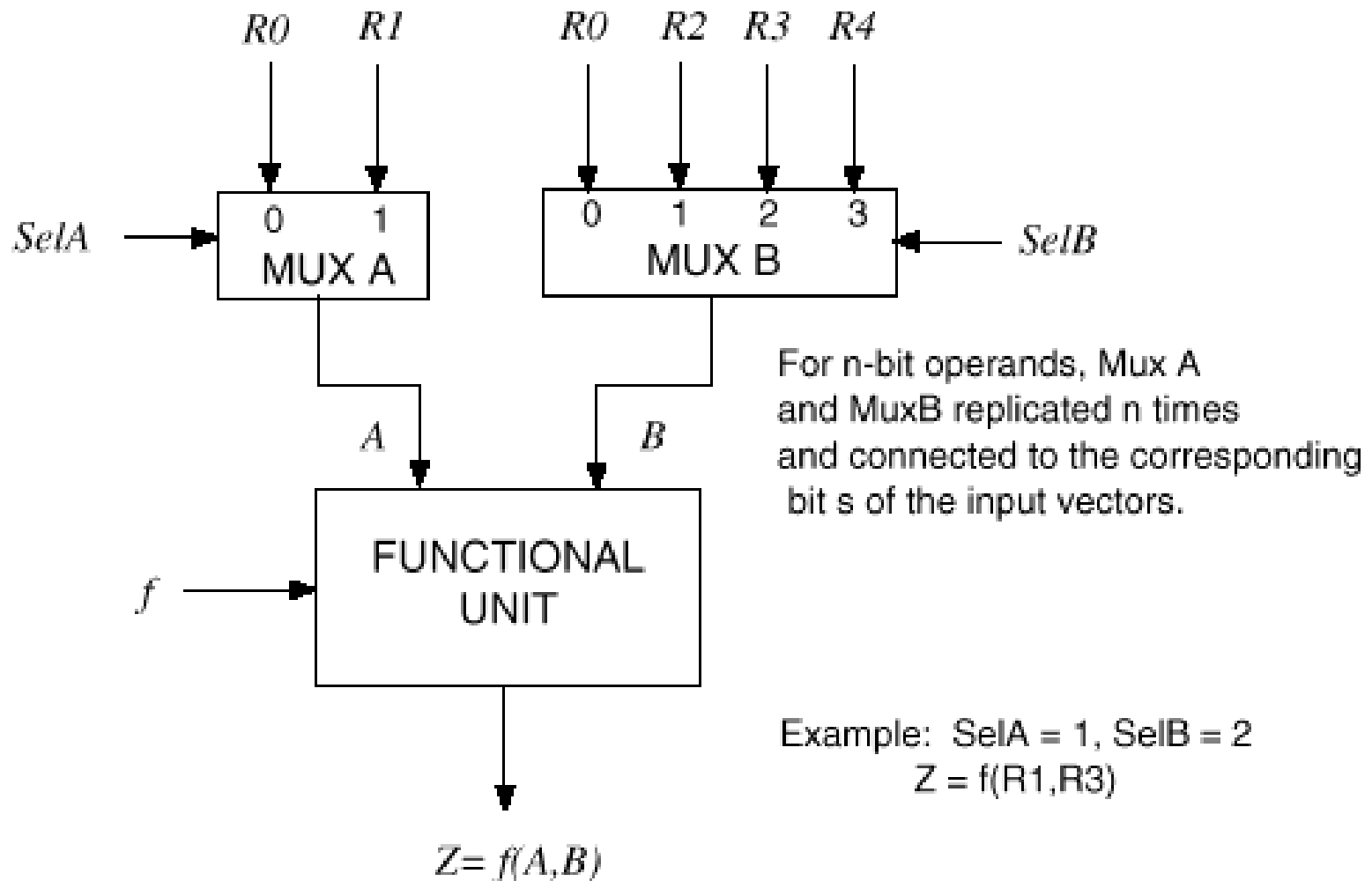


Figure 9.21: Multiplexer example of use.
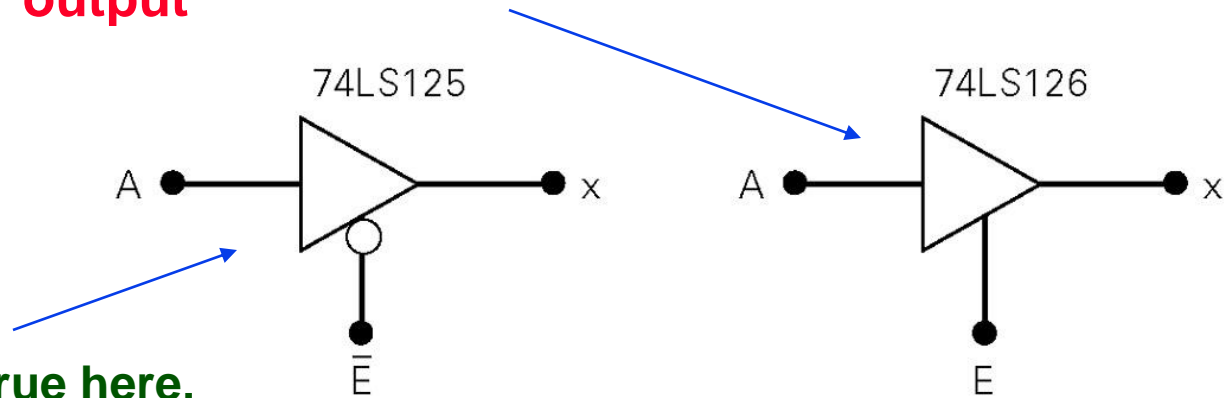
# Three-state gates

- A multiplexer can be constructed with three-state gates
- Output state: 0, 1, and high-impedance (open ckts)
- If the select input (E) is 0, the three-state gate has **no output**



**Opposite true here,  
No output if  $\bar{E}$  is 1**

$\bar{E}$	x
0	A
1	Hi-Z


(a)

E	x
0	Hi-Z
1	A


(b)
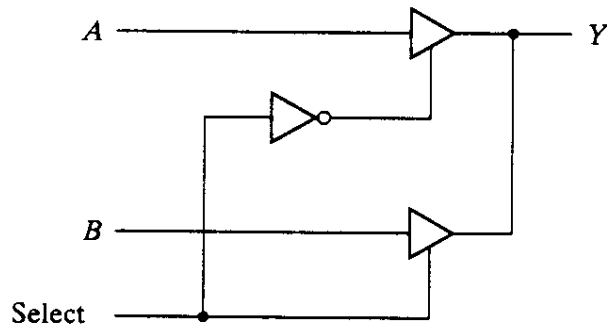
# Three-state gates

- A multiplexer can be constructed with three-state gates
- Output state: 0, 1, and high-impedance (open cks)
- If the select input is low, the three-state gate has **no output**



(a) 2-to-1- line mux

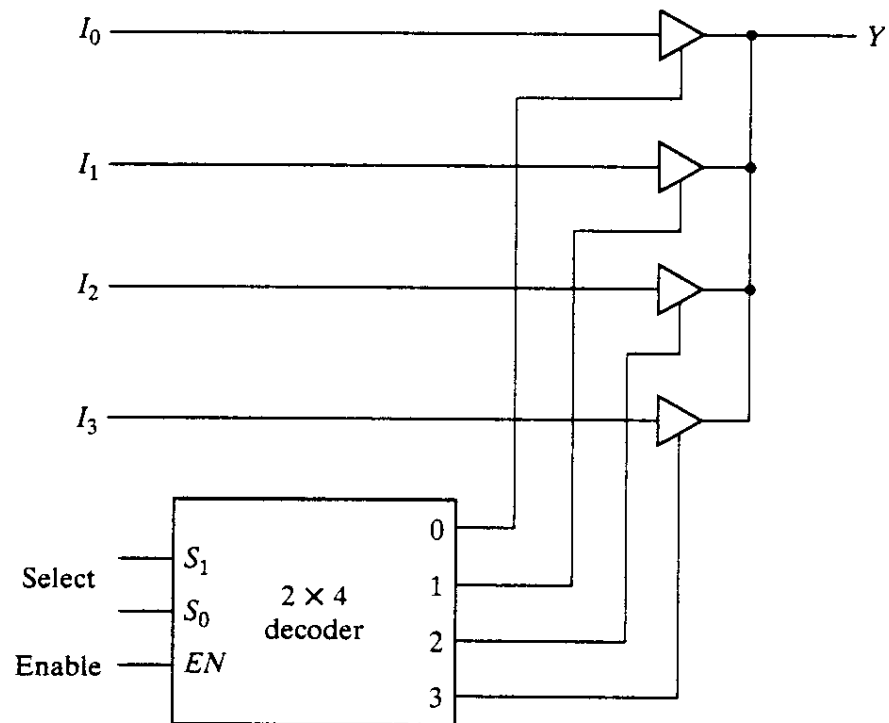

(b) 4 - to - 1 line mux



# Summary

- **Magnitude comparators allow for data comparison**
  - Can be built using and-or gates
- **Greater/less than requires more hardware than equality**
- **Multiplexers are fundamental digital components**
  - Can be used for logic
  - Useful for **datapaths**
  - Scalable
- **Tristate buffers have three types of outputs**
  - 0, 1, high-impedence (Z)
  - Useful for datapaths