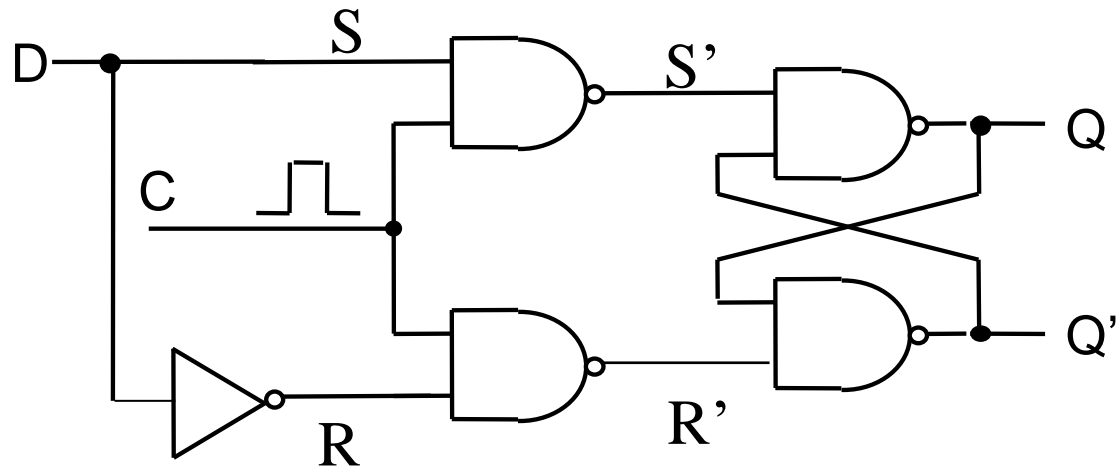


Sequential Circuits: Flip flops

Overview

- Latches respond to trigger **levels** on control inputs
 - Example: If $G = 1$, input reflected at output
- Difficult to precisely time when to store data with latches
- **Flip flops** store data on a **rising** or **falling** trigger edge.
 - Example: control input transitions from 0 -> 1, data input appears at output
 - Data remains stable in the flip flop until until next rising edge.
- Different types of flip flops serve different functions
- Flip flops can be defined with **characteristic functions**.

D Latch



D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q_0	Q_0'


S	R	C	Q	Q'	
0	0	1	Q_0	Q_0'	Store
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	1	1	Disallowed
X	X	0	Q_0	Q_0'	Store

- When C is high, D passes from input to output (Q)

Clocking Event

- What if the output only changed on a **C transition**?


Positive edge triggered

 

D	C	Q	Q'
0	↑	0	1
1	↑	1	0
X	0	Q_0	Q_0'



Hi-Lo edge

 

Lo-Hi edge

Master-Slave D Flip Flop

- Consider two latches combined together
- Only one C value active at a time
- Output changes on **falling** edge of the clock


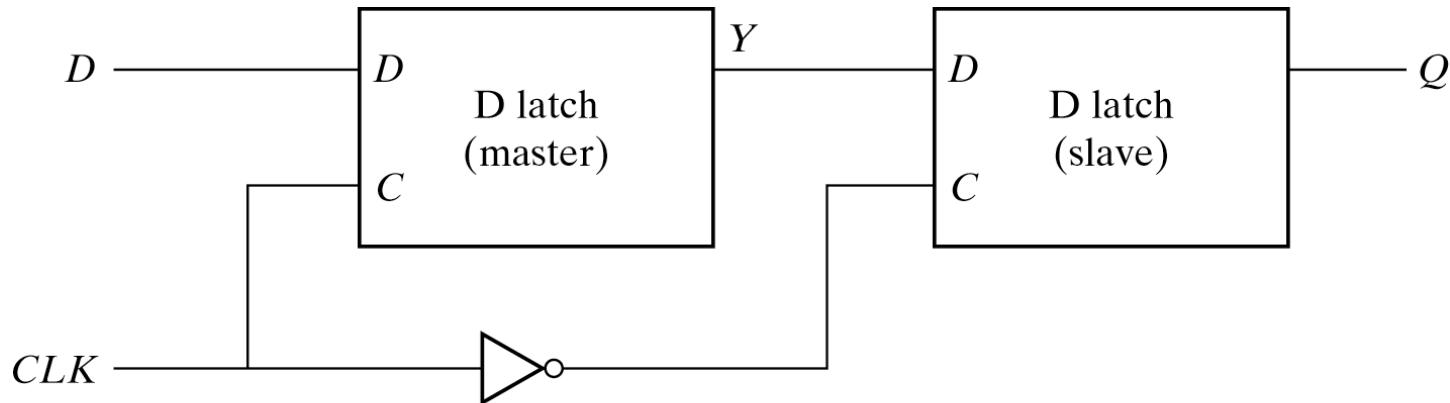


Fig. 5-9 Master-Slave D Flip-Flop

D Flip-Flop

- Stores a value on the positive edge of **C**
- Input changes at other times have no effect on output

Positive edge triggered


 


D	C	Q	Q'
0	↑	0	1
1	↑	1	0
X	0	Q_0	Q_0'

D gets latched to Q on the rising edge of the clock.


Clocked D Flip-Flop

  - Stores a value on the positive edge of **C**
- Input changes at other times have no effect on output




Positive and Negative Edge D Flip-Flop

 - D flops can be triggered on positive or negative edge
- Bubble before **Clock (C)** input indicates **negative edge trigger**



(a) Positive-edge

 

(a) Negative-edge

Fig. 5-11 Graphic Symbol for Edge-Triggered *D* Flip-Flop




Lo-Hi edge




Hi-Lo edge

Positive Edge-Triggered J-K Flip-Flop

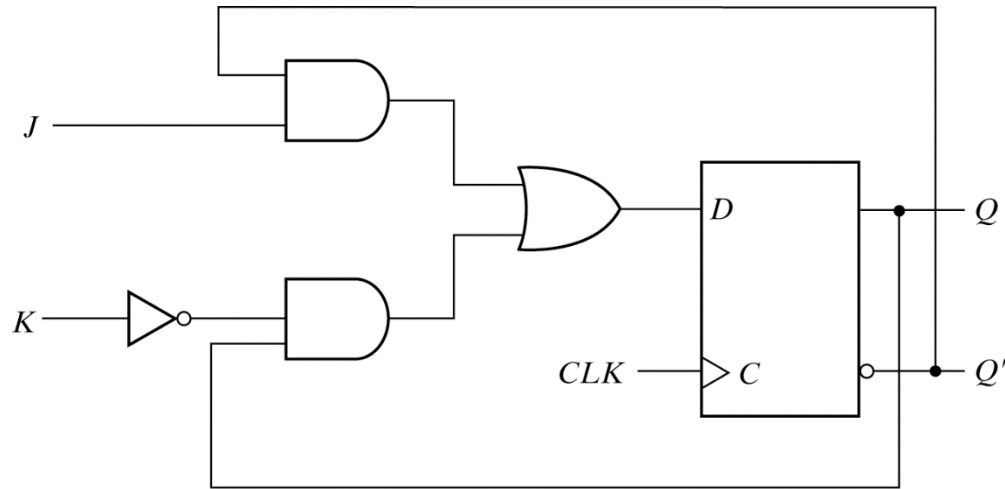

(a) Circuit diagram

 

(b) Graphic symbol

Fig. 5-12 JK Flip-Flop

°Created from D flop

°J sets

°K resets


°J=K=1 -> invert output

J	K	CLK	Q	Q'
0	0		Q_0	
0	1		0	
1	0		1	
1	1		TOGGLE	

Q_0'
1
0

Clocked J-K Flip Flop

 
- Two data inputs, **J** and **K**
- J** -> set, **K** -> reset, if **J=K=1** then toggle output



J	K	CLK	Q
0	0	\uparrow	Q_0 (no change)
1	0	\uparrow	1
0	1	\uparrow	0
1	1	\uparrow	\bar{Q}_0 (toggles)


(a)

Characteristic Table

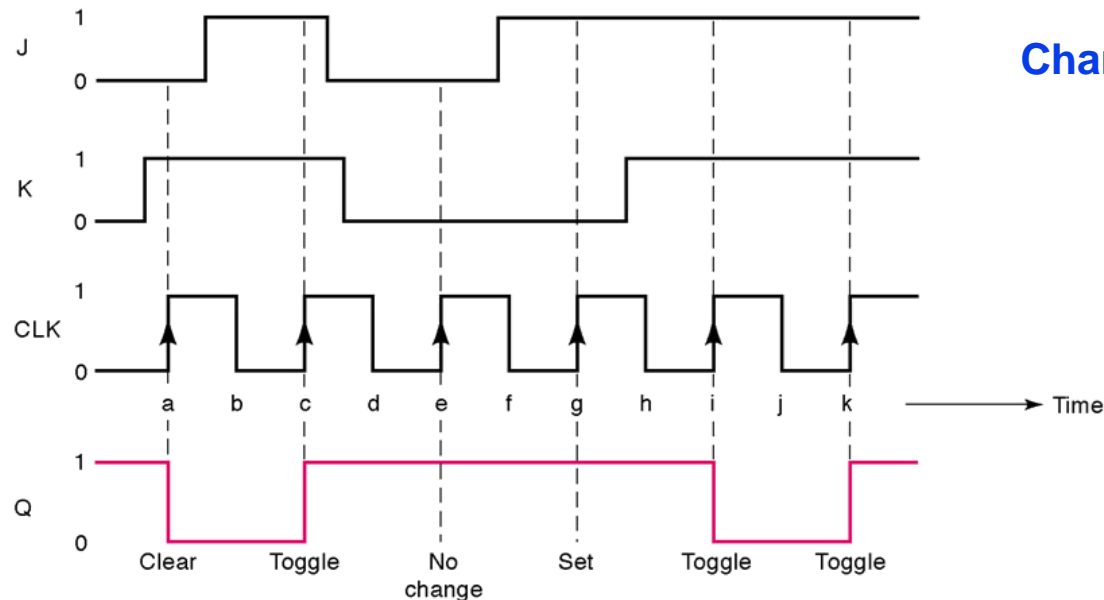


(b)


Positive Edge-Triggered T Flip-Flop

 

(a) From *JK* flip-flop

 

(b) From *D* flip-flop

 

(c) Graphic symbol

Fig. 5-13 T Flip-Flop

° Created from D flop

° $T=0 \rightarrow$ keep current

° K resets


° $T=1 \rightarrow$ invert current

T	C	Q	Q'
	0	Q_0	
	1	TOGGLE	

Q_0'

Asynchronous Inputs

 
- J, K are **synchronous inputs**
 - o Effects on the output are synchronized with the *CLK* input.
- **Asynchronous inputs** operate independently of the synchronous inputs and clock
 - o Set the FF to 1/0 states *at any time*.



PRESET	CLEAR	FF response
1	1	Clocked operation*
0	1	Q = 1 (regardless of CLK)
1	0	Q = 0 (regardless of CLK)
0	0	Not used

*Q will respond to J, K, and CLK


Asynchronous Inputs

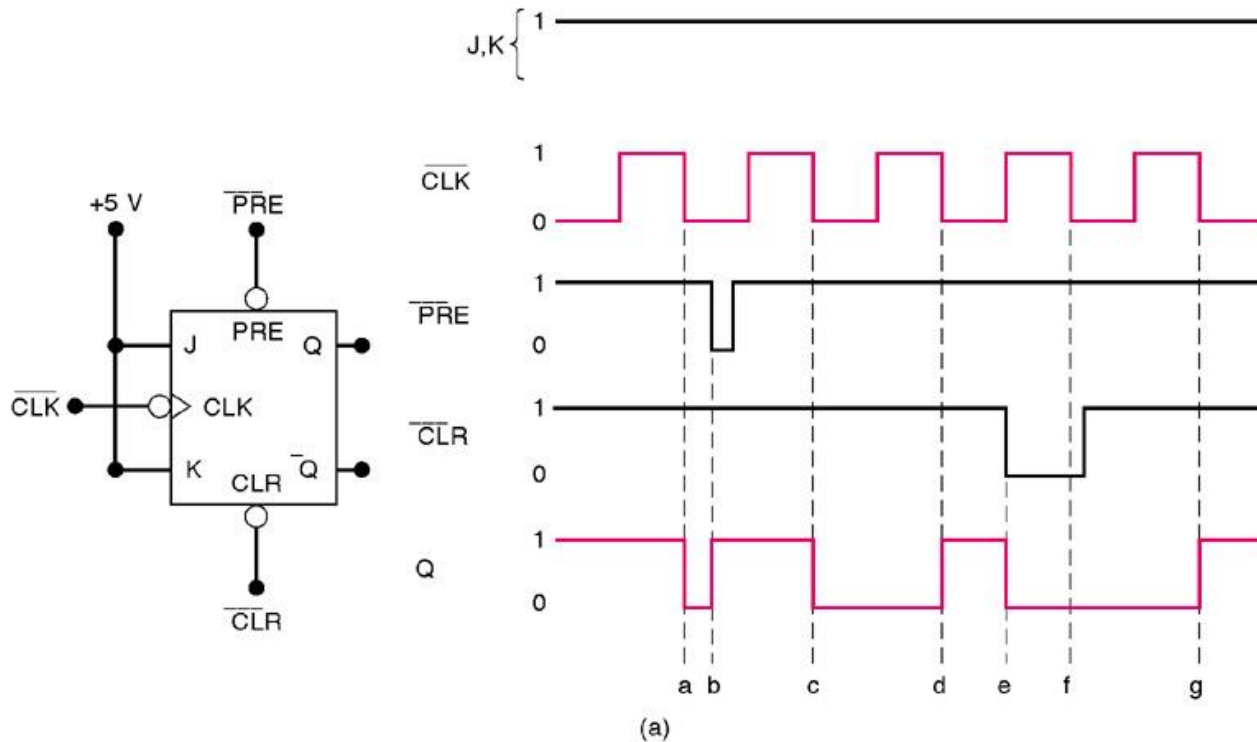

Point	Operation
a	Synchronous toggle on NGT of CLK
b	Asynchronous set on $\overline{PRE} = 0$
c	Synchronous toggle
d	Synchronous toggle
e	Asynchronous clear on $\overline{CLR} = 0$
f	\overline{CLR} over-rides the NGT of CLK
g	Synchronous toggle


(b)

Asynchronous Inputs

 

 (a) Circuit diagram

- Note reset signal (R) for D flip flop
- If $R = 0$, the output Q is cleared
- This event can occur at any time, regardless of the value of the CLK



(b) Graphic symbol


R	C	D	Q	Q'
0	X	X	0	1
1	\uparrow	0	0	1
1	\uparrow	1	1	0

(b) Function table

Fig. 5-14 D Flip-Flop with Asynchronous Reset

Parallel Data Transfer

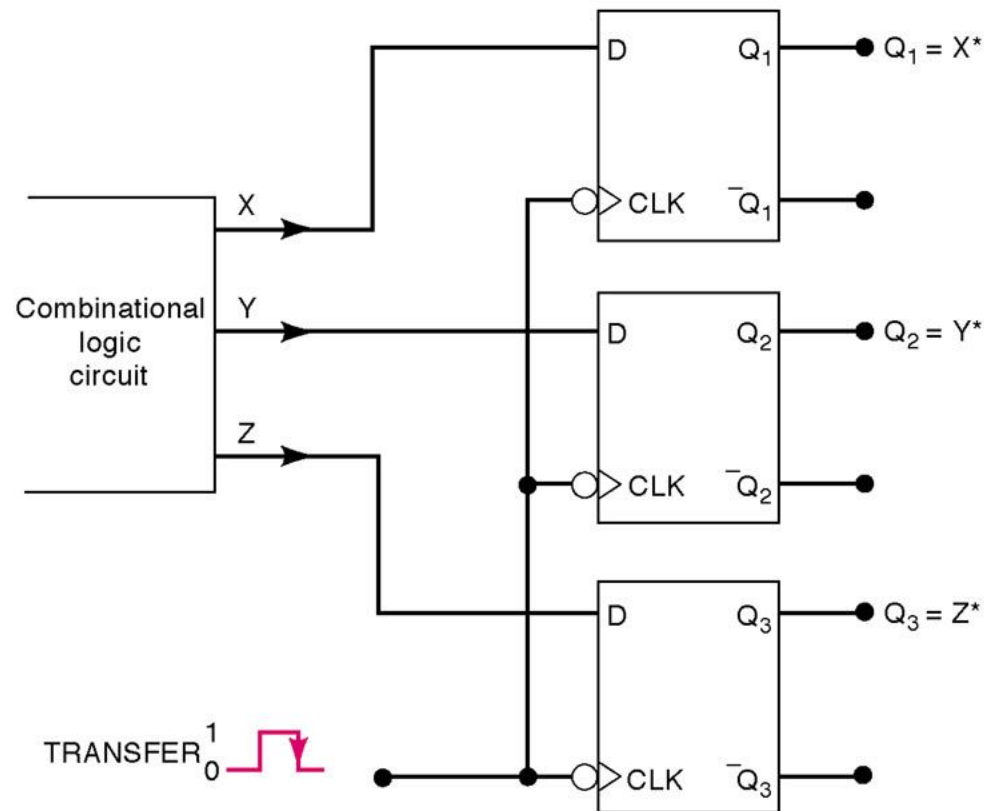- Flip flops store outputs from combinational logic
- Multiple flops can store a collection of data



*After occurrence of NGT

Summary

- Flip flops are powerful storage elements
 - They can be constructed from gates and latches!
- D flip flop is simplest and most widely used
- Asynchronous inputs allow for clearing and presetting the flip flop output
- Multiple flops allow for data storage
 - The basis of computer **memory**!
- Combine storage and logic to make a computation circuit
- Next time: Analyzing sequential circuits.